

TTK4240 Industriell elektroteknikk

January 14, 2025

Marta Molinas

Institutt for teknisk kybernetikk

Lecture - Week 35 – Part II

**Review of Low-Pass
and High-Pass Filters**

&

**Instantaneous &
Average Power in brief**

- **Bandpass Filters**
 - Center Frequency, Bandwidth and Quality Factor
 - Series RLC
- **Bandreject Filters**
 - Series RLC
 - Transfer Function

Nilsson's Book Chapter 14: 14.1 to 14.5


Review of the low-and high-pass Filters

Passive Filter

Review

Definition

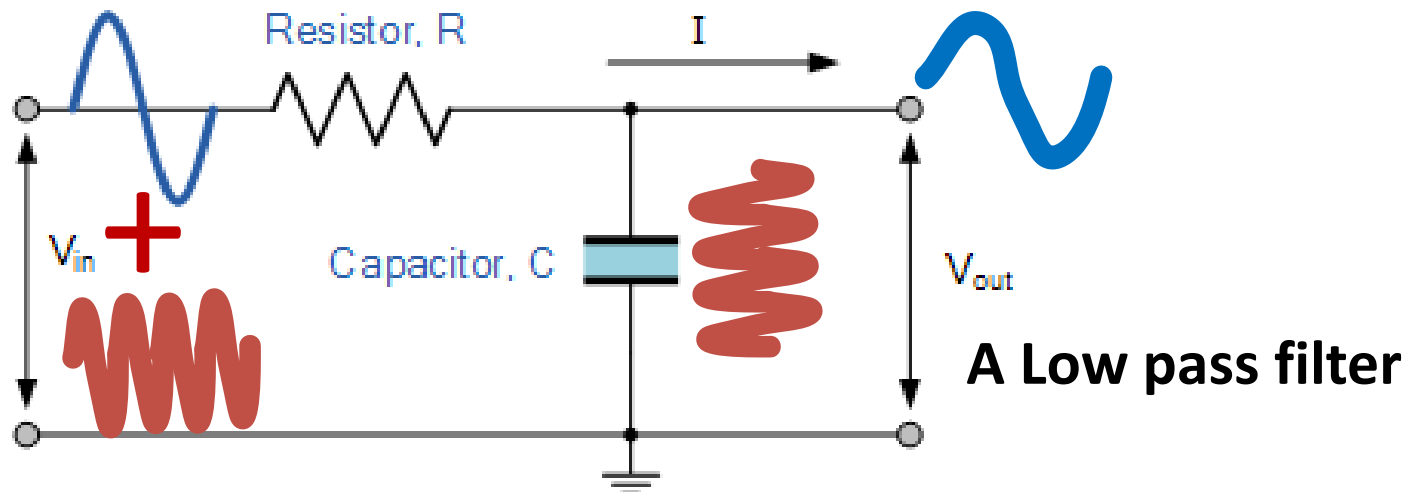The passive filter is a *frequency-dependent circuit* that can *selectively pass* signals at certain frequencies, while attenuates the signals at other frequencies.




Key point for filter design

We need some frequency-dependent **circuit elements**, so that we can use their frequency-dependent **properties** to design a frequency **selective circuit**.

L and C

$$Z_L(j\omega) = j\omega L$$

$\omega = 0$
(Low frequency)

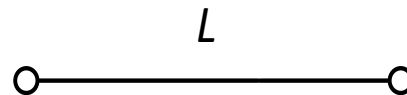


Pass

$\omega = \infty$
(High frequency)




Block

$$Z_C(j\omega) = \frac{1}{j\omega C}$$

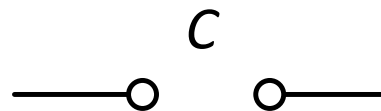


Block

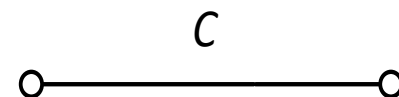

Pass

The Cutoff Frequency ω_c *for practical passive filters*

Review

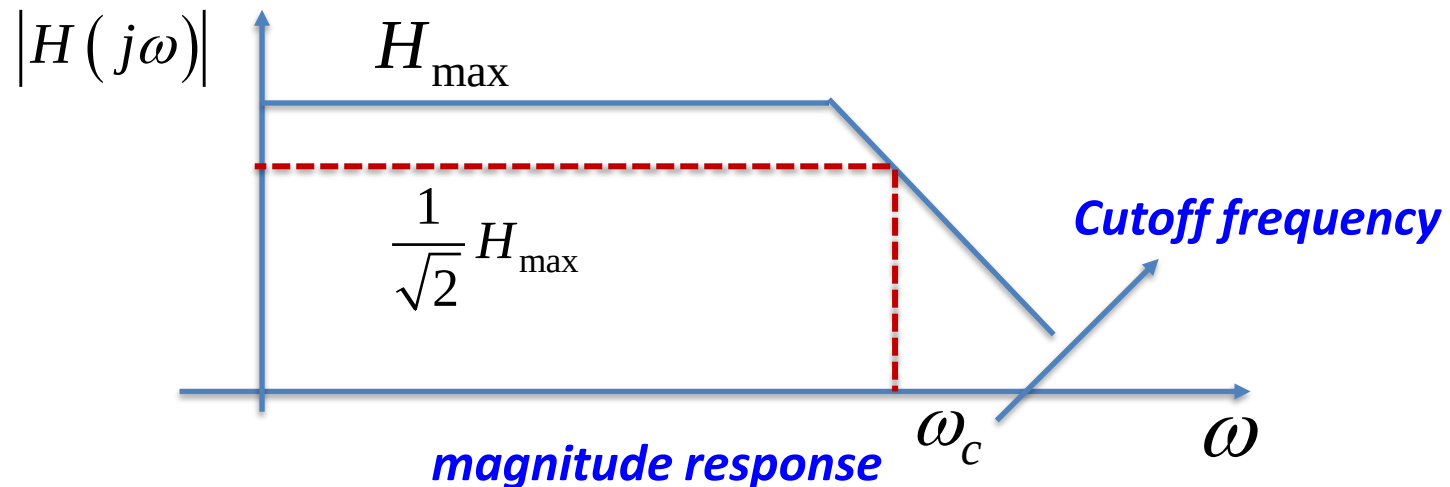

- The cutoff frequency is the frequency at which the magnitude of the transfer function equals:

$$\left(1/\sqrt{2}\right)H_{\max}$$

The physical meaning of cutoff frequency: *a power perspective*

Review

$$\begin{aligned}|V_L(j\omega_c)| &= |H(j\omega_c)||V_i| \\ &= \frac{1}{\sqrt{2}} H_{\max}|V_i| \\ &= \frac{1}{\sqrt{2}} V_{L\max}.\end{aligned}$$



$$\begin{aligned}P(j\omega_c) &= \frac{1}{2} \frac{|V_L^2(j\omega_c)|}{R} \\ &= \frac{1}{2} \frac{\left(\frac{1}{\sqrt{2}} V_{L\max}\right)^2}{R} \\ &= \frac{1}{2} \frac{V_{L\max}^2/2}{R} \\ &= \frac{P_{\max}}{2}.\end{aligned}$$


- The Cutoff Frequency is the frequency at which the *power transfer to the output is reduced to half!*



Check 14.2 Defining the cutoff frequency, page 525

Instantaneous Power (10.1 Nilsson)

Hand notes

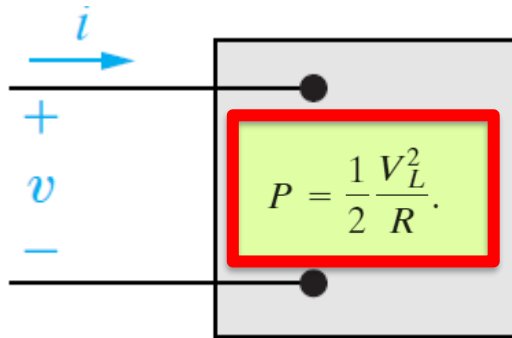

$$v = V_m \cos(\omega t + \theta_v),$$

$$i = I_m \cos(\omega t + \theta_i),$$

Instantaneous power is defined as

$$p = vi.$$

$$p = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

Check also 10.3 for a simpler calculation through RMS value, page 366

Use this Trigonometric Identity

$$\cos \alpha \cos \beta = \frac{1}{2} \cos (\alpha - \beta) + \frac{1}{2} \cos (\alpha + \beta)$$

$$p = V_m I_m \cos(\underbrace{\omega t + \theta_v}_{\alpha}) \cos(\underbrace{\omega t + \theta_i}_{\beta})$$



$$p = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(2\omega t + \theta_v + \theta_i)$$

Redefine the time at which the current phase crosses zero, i.e. $\omega t = \omega \tau - \theta_i$

$$p = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(2\omega \tau + \theta_v - \theta_i)$$

$$\cos(\alpha + \beta) = \cos \alpha \cos \beta - \sin \alpha \sin \beta$$

Resubstitute
 $\tau = t$

$$p = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(2\omega t + \theta_v - \theta_i)$$



$$p = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \cos(2\omega t) - \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \sin(2\omega t)$$

constant

sinusoidal

Average and Reactive Power

$$p = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \cos 2\omega t - \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \sin 2\omega t.$$

$$p = P + P \cos 2\omega t - Q \sin 2\omega t,$$

$$P = \frac{1}{T} \int_{t_0}^{t_0+T} p \, dt, \quad \text{Average value}$$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i),$$


Active power

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i).$$

Reactive power

Defined
as P or
average
power

Power for purely resistive circuits

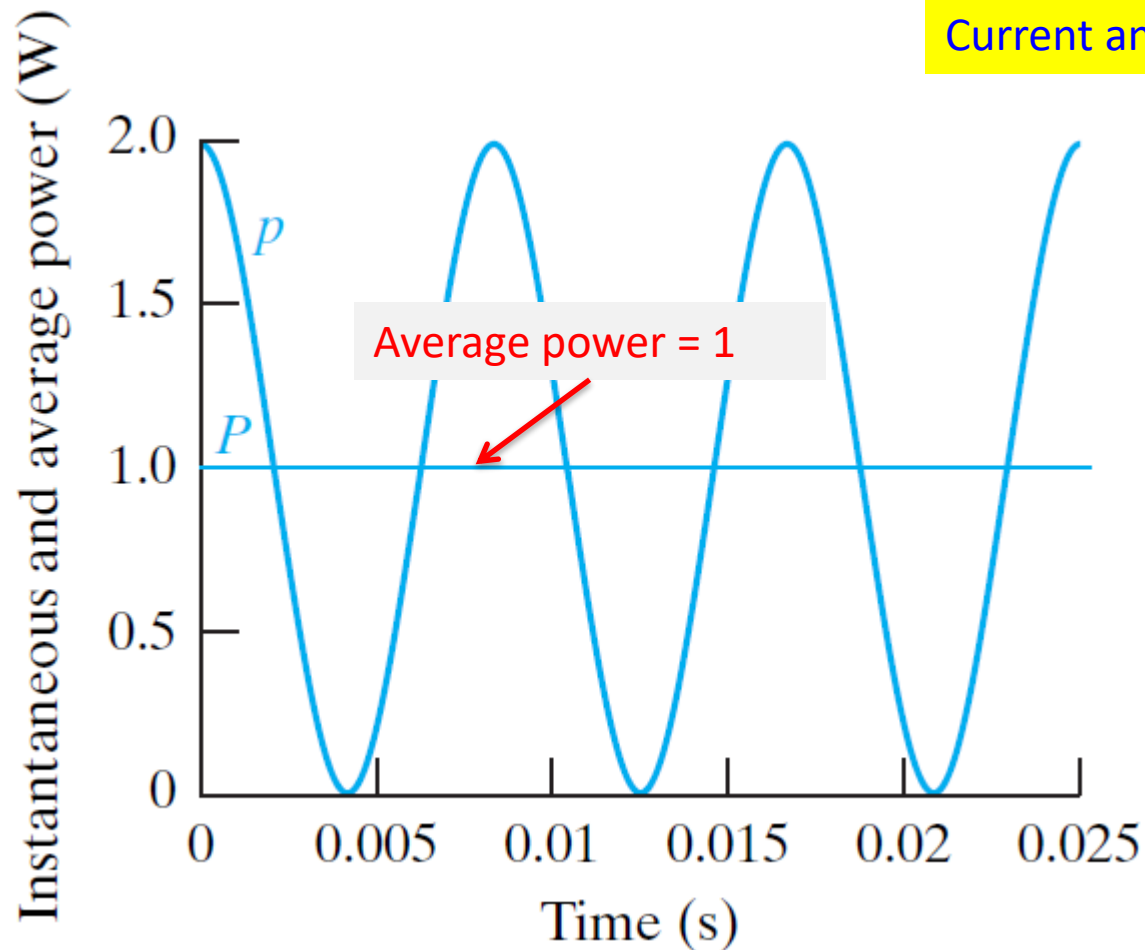



Current and voltage are in phase

$$\theta_v = \theta_i.$$

$$p = P + P \cos 2\omega t.$$

Low-Pass Filters: *RL*-based

Review

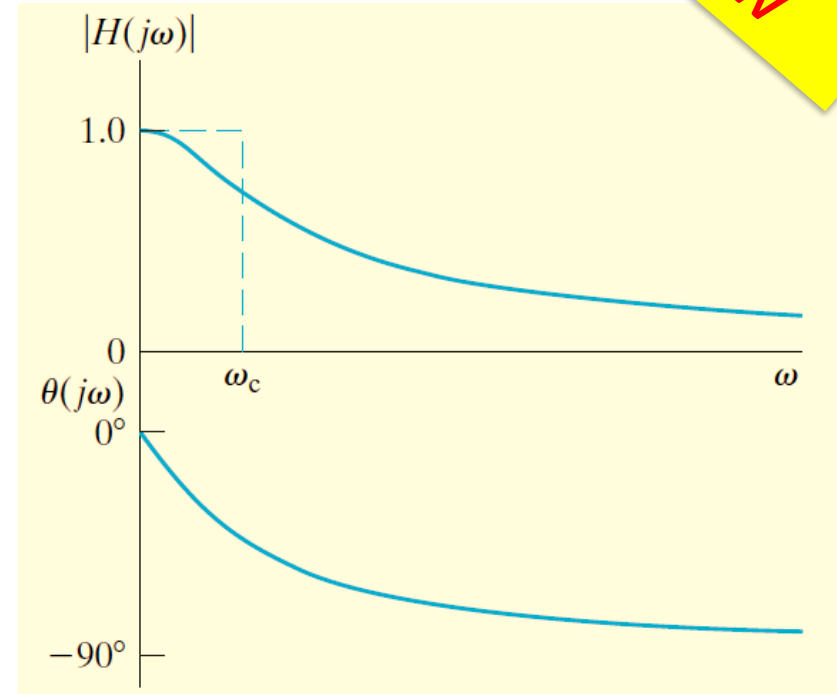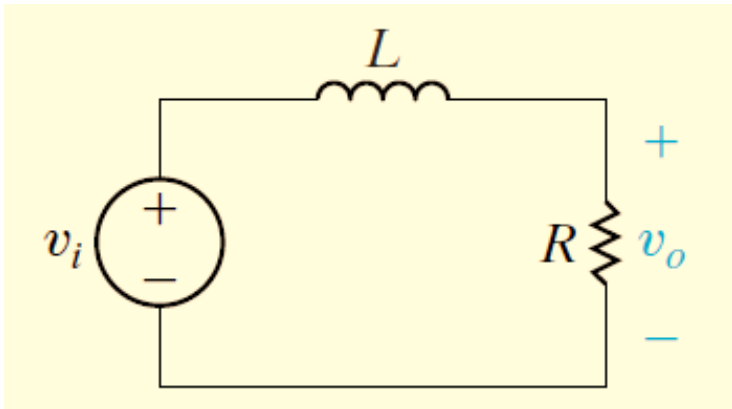

$$|H(j\omega)| = \frac{R/L}{\sqrt{\omega^2 + (R/L)^2}},$$

Cut off frequency



$$\theta(j\omega) = -\tan^{-1}\left(\frac{\omega L}{R}\right).$$

Im
Re

$$\omega_c = \frac{R}{L}$$

Low-Pass Filters: **RC-based**

Review

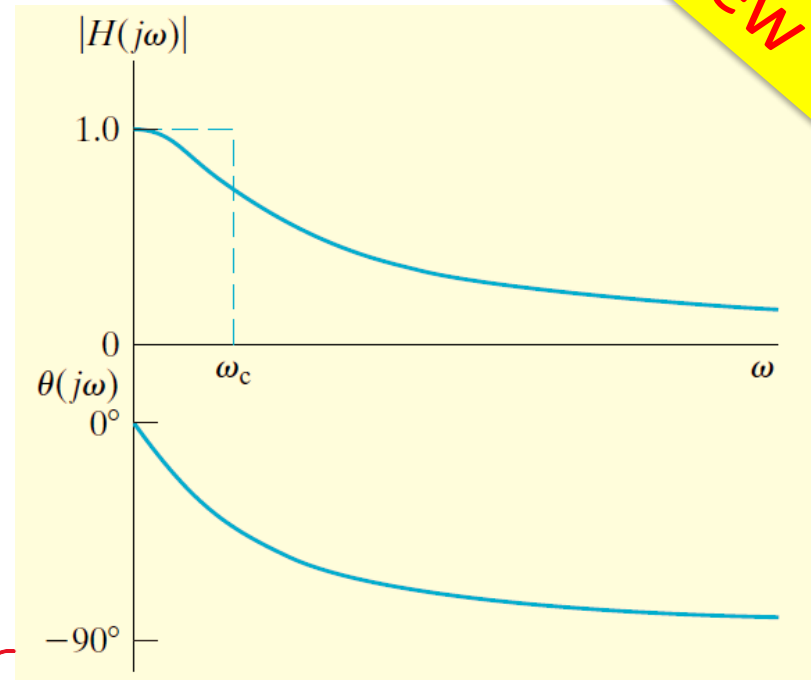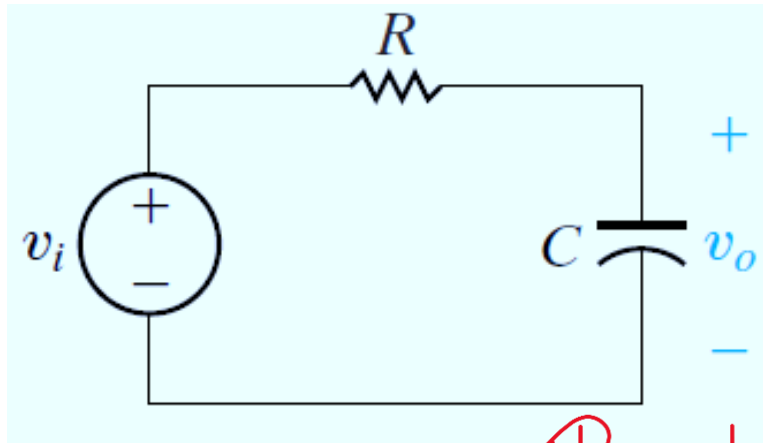

$$|H(j\omega)| = \frac{1/RC}{\sqrt{\omega^2 + (1/RC)^2}}$$

Real number

$$\theta(j\omega) = -\tan^{-1} \frac{\omega}{1/RC} = -\frac{y}{x}$$


Cut off frequency

$$\omega_c = \frac{1}{RC}$$


Low-pass filter comparison

Review

RL type

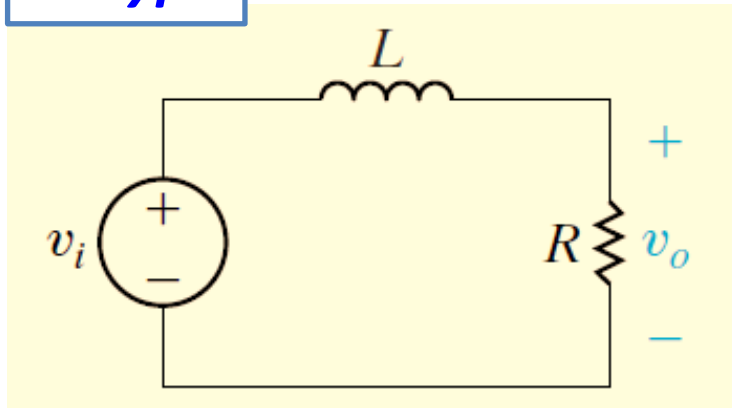

RC type

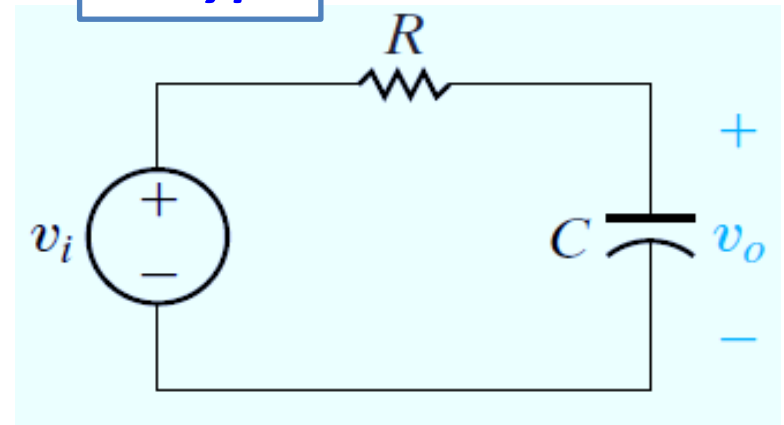

$$\omega_c = \frac{R}{L}$$

$$\omega_c = \frac{1}{RC}$$


$$H(s) = \frac{\omega_c}{s + \omega_c}$$

First-order low pass filter

*Maximum order of polynomials is **ONE***


High-Pass Filters: *RC type*

Review

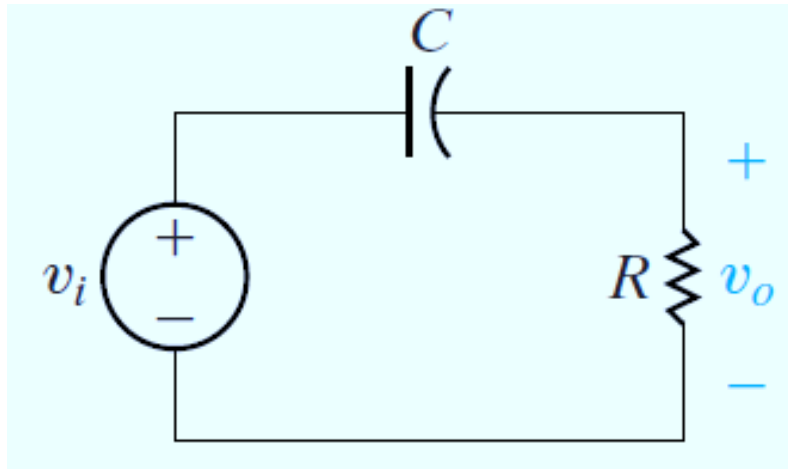


$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{s}{s + 1/RC}$$

$$|H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + (1/RC)^2}},$$

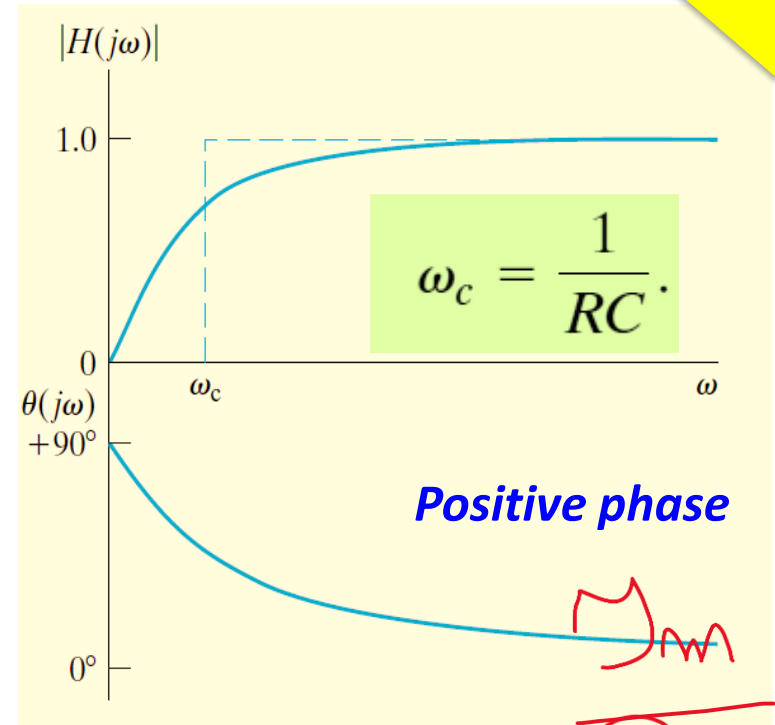


$$\theta(j\omega) = 90^\circ - \tan^{-1} \omega RC.$$

High-Pass Filters: *RL* type

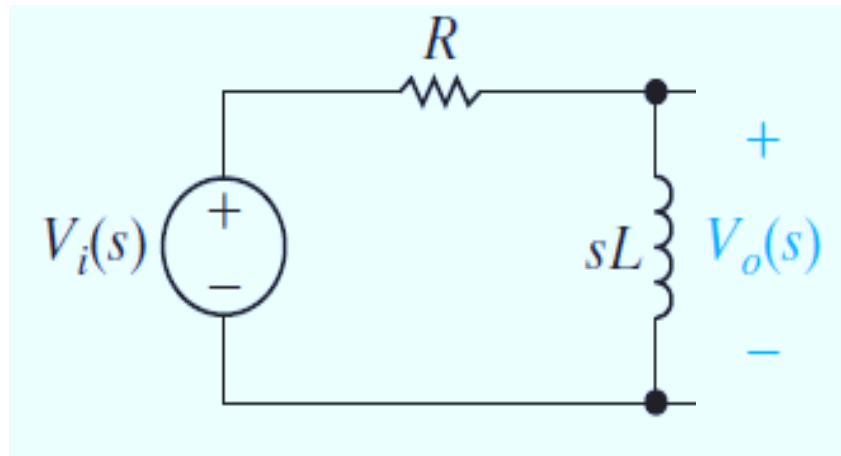

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{sL}{R + sL}$$


$$|H(j\omega)| = \frac{\omega}{\sqrt{(R/L)^2 + \omega^2}}$$

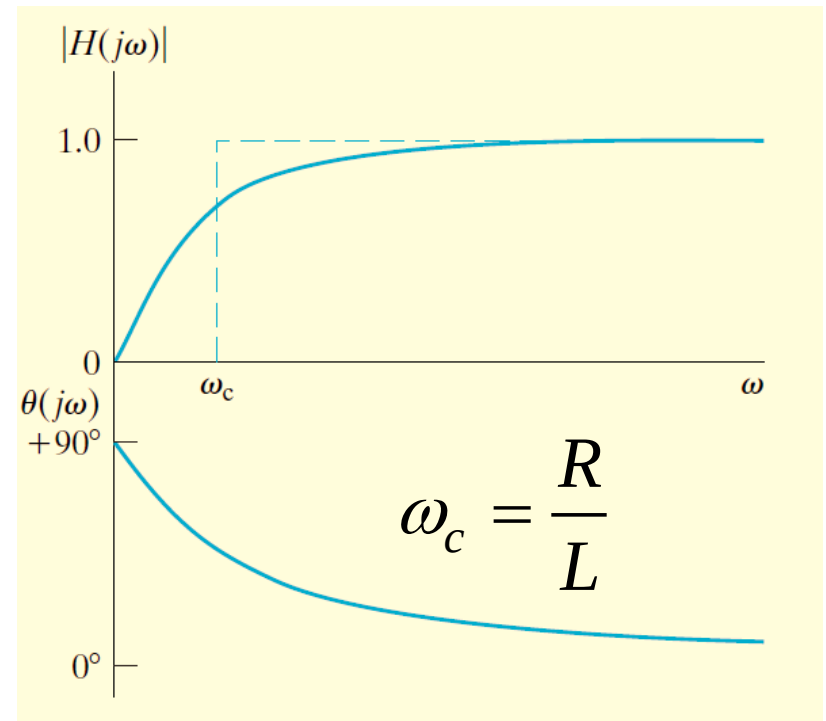


$$\theta(j\omega) = 90^\circ - \tan^{-1} \frac{\omega}{R/L}$$

High-pass filter comparison

RL type

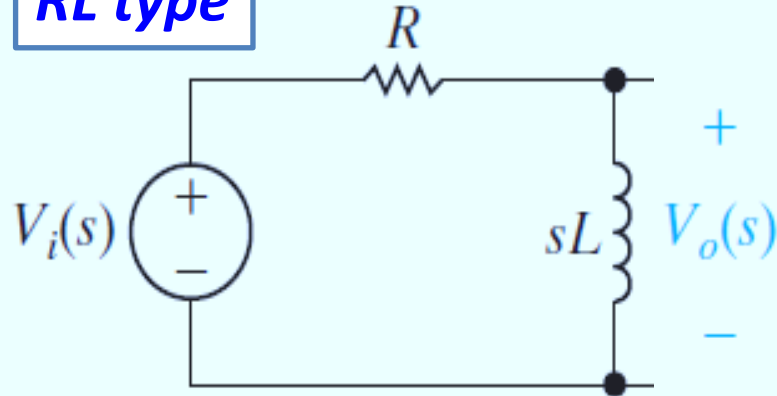

RC type

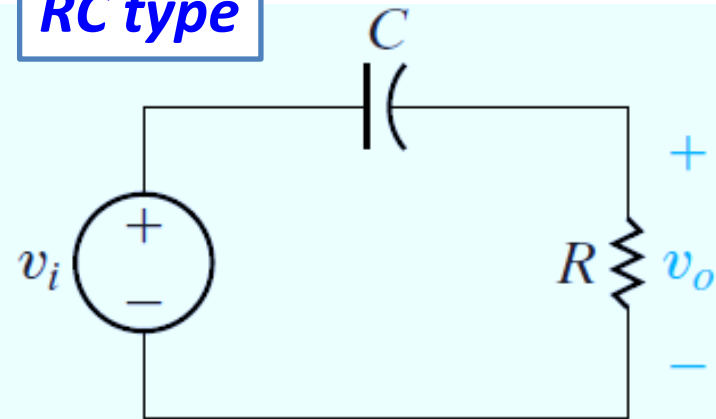

$$\omega_c = \frac{R}{L}$$


$$\omega_c = \frac{1}{RC}$$

$$H(s) = \frac{s}{s + \omega_c}$$

First-order high pass filter

*Maximum order of polynomials is **ONE***

Loaded passive filters

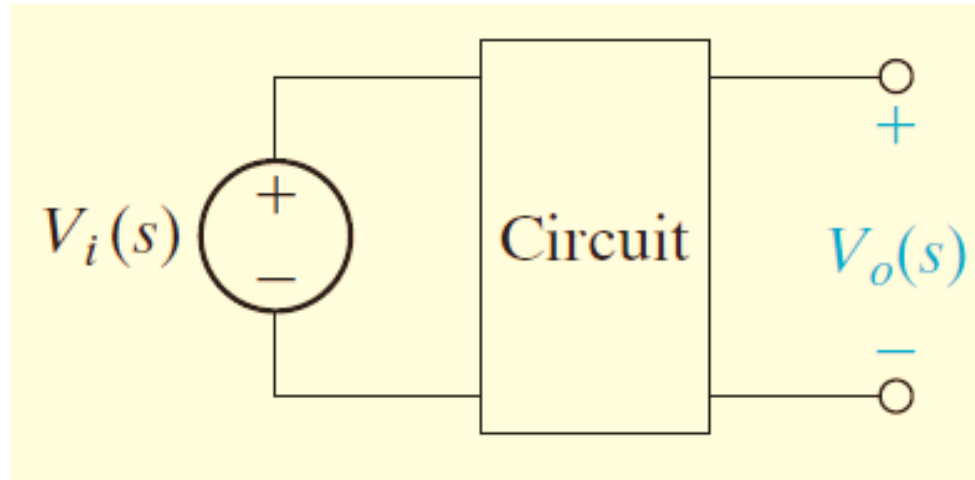



Problem:

If the filter's output is connected to other elements, like a resistive load, what will happen ?

And, will it affect the performance of the filter?

Example:

Ex. 14.3 & 14.4 (Nilsson)

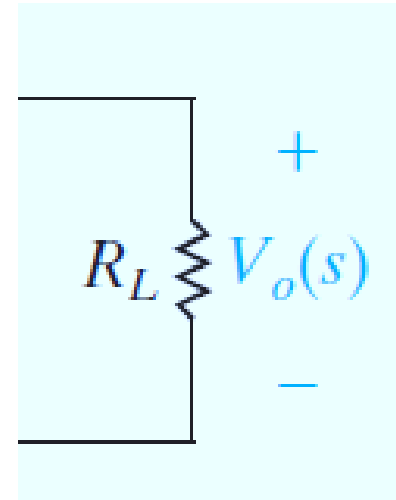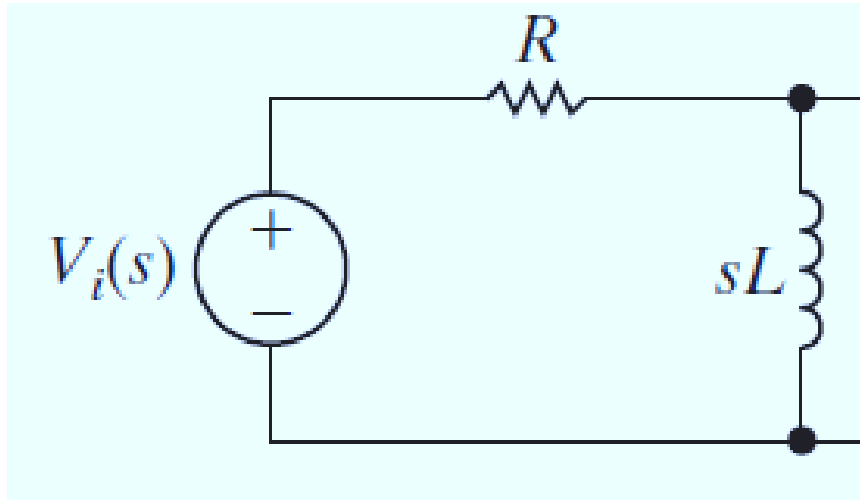

$$V_{out}(s) = \frac{R_L // sL}{R + \boxed{R_L // sL}} V_{in}(s) \quad \xrightarrow{\text{red arrow}} \quad R_L // sL = \frac{R_L \cdot sL}{R_L + sL}$$

Transfer function of the loaded filter

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{s \frac{R_L}{R_L + R}}{s + \frac{R}{L} \frac{R_L}{R_L + R}}$$

$$K = \frac{R_L}{R_L + R}$$

$$\omega_c = K \frac{R}{L}$$




$$H(s) = \frac{sK}{s + \omega_c}$$

Frequency response

$$s = j\omega$$

$$|H(j\omega)| = \frac{\omega K}{\sqrt{\omega^2 + \omega_c^2}}$$
$$\angle H(j\omega) = \frac{\pi}{2} - \tan^{-1} \frac{\omega}{\omega_c}$$

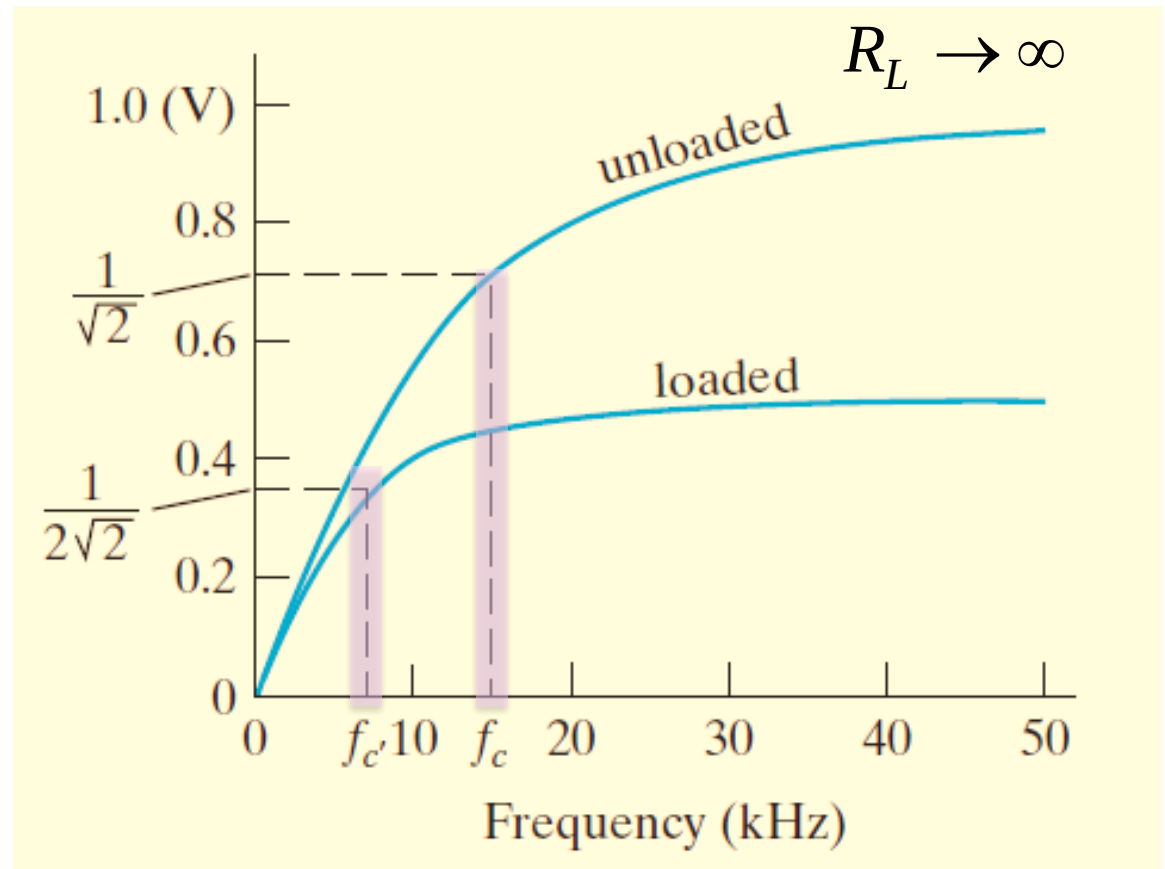


$$K = \frac{R_L}{R_L + R}$$

$$K < 1$$


$$R_L \rightarrow \infty, K \approx 1$$

Output signals are *degraded* under the loaded filter

Amplifier*

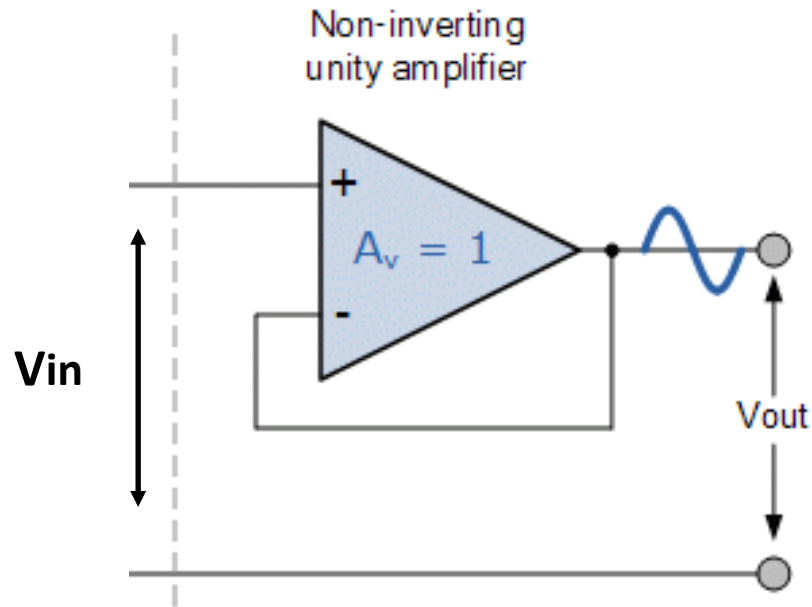


Amplifier

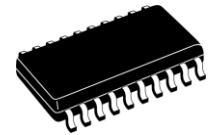


Two features

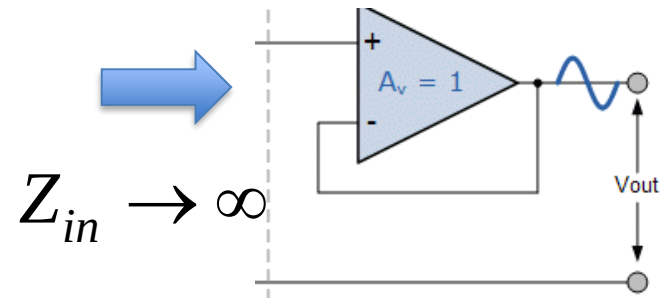- $V_{in} \approx V_{out}$
- $Z_{in} \rightarrow \infty$




*supplementary contents

Active filters*

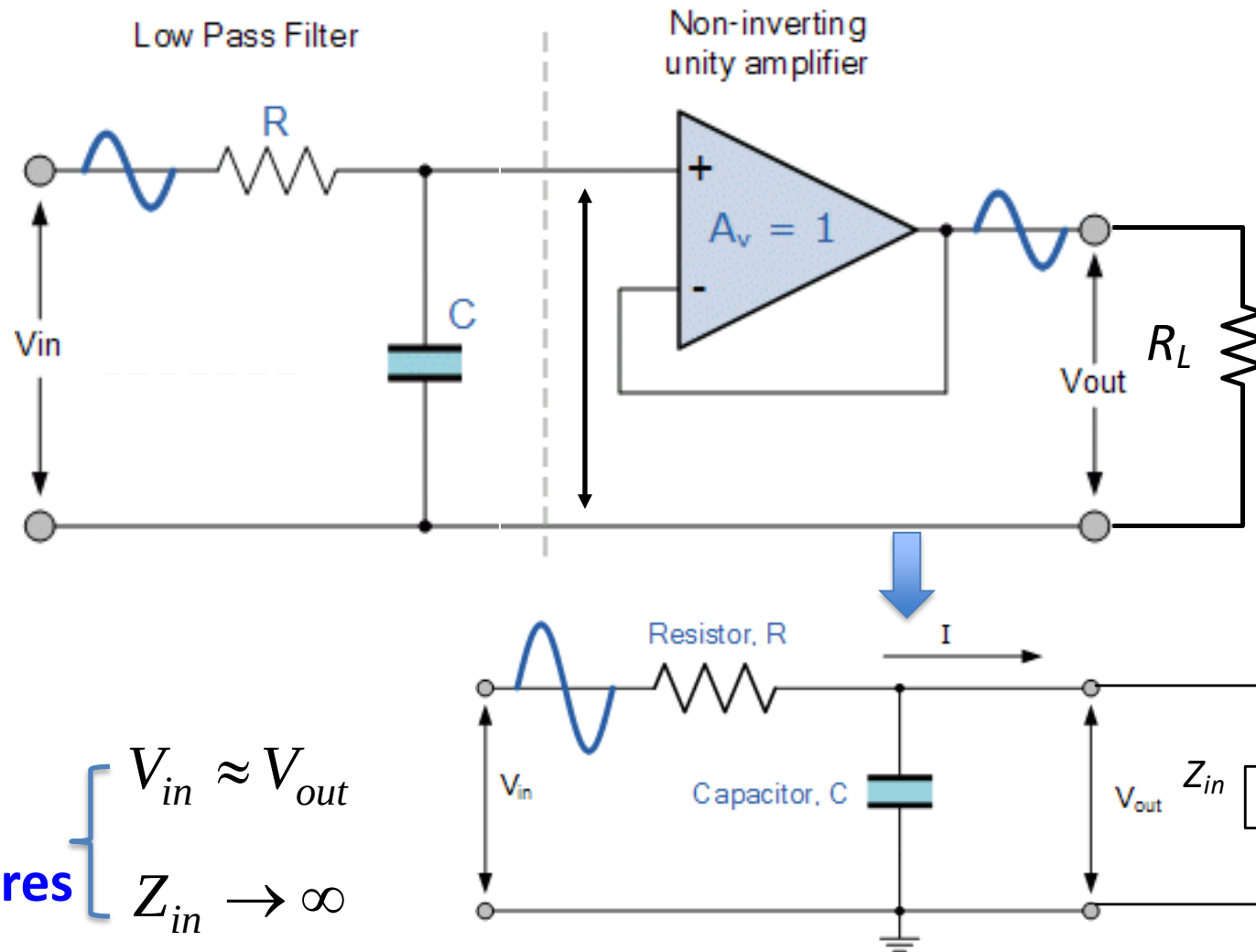

*supplementary contents

Active filter*

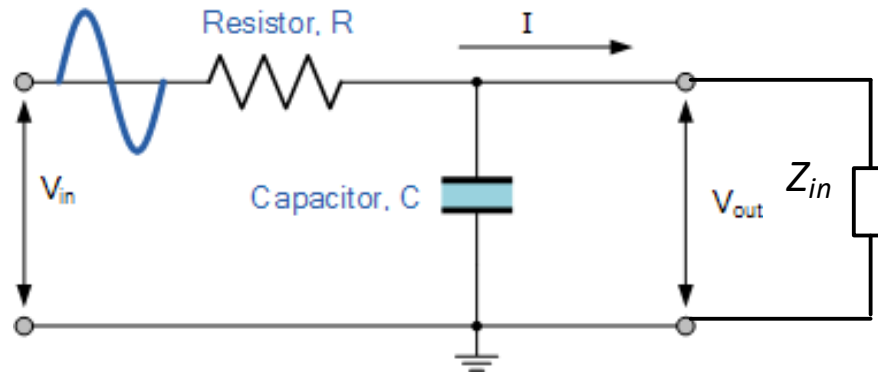

$$H(s) = \frac{V_{out}}{V_{in}} = \frac{Z_{in} // \frac{1}{sC}}{R + Z_{in} // \frac{1}{sC}} \approx \frac{\frac{1}{sC}}{R + \frac{1}{sC}}$$

The active filter can assure the performance of passive filter regardless of the **load variation**



*supplementary contents

Break

Bandpass filter


Hand notes

Band-pass or -reject filters

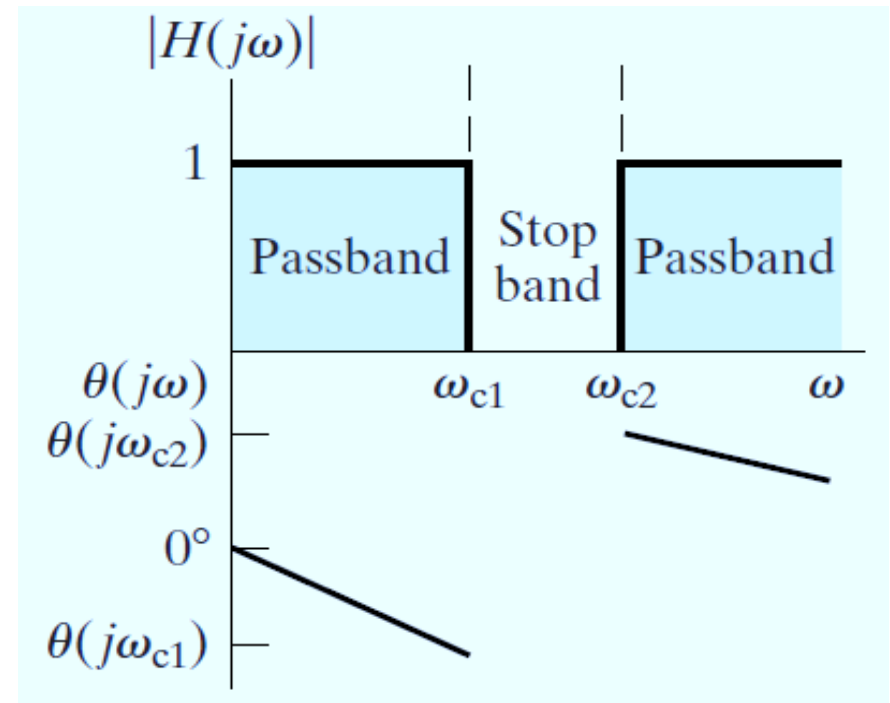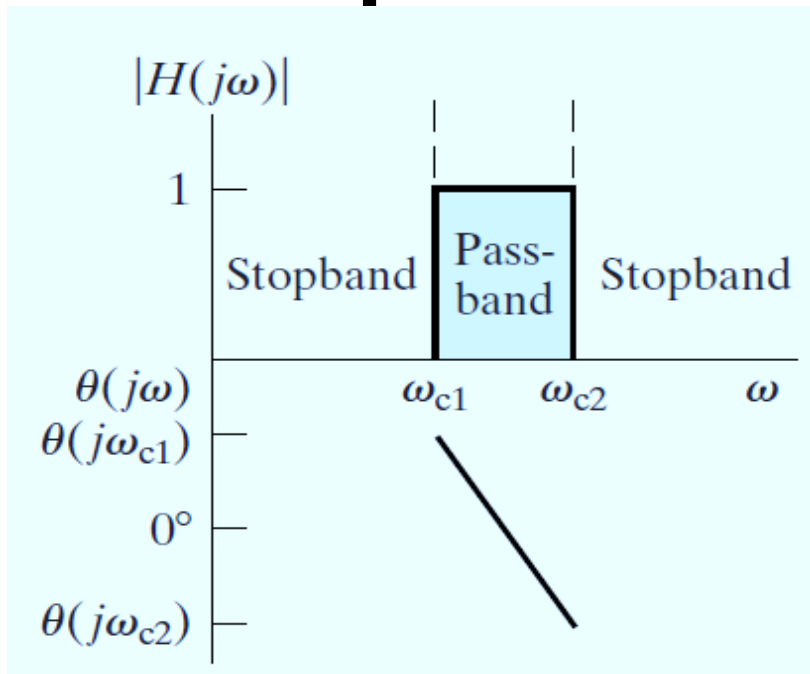

*Shape of magnitude response changes **TWICE***

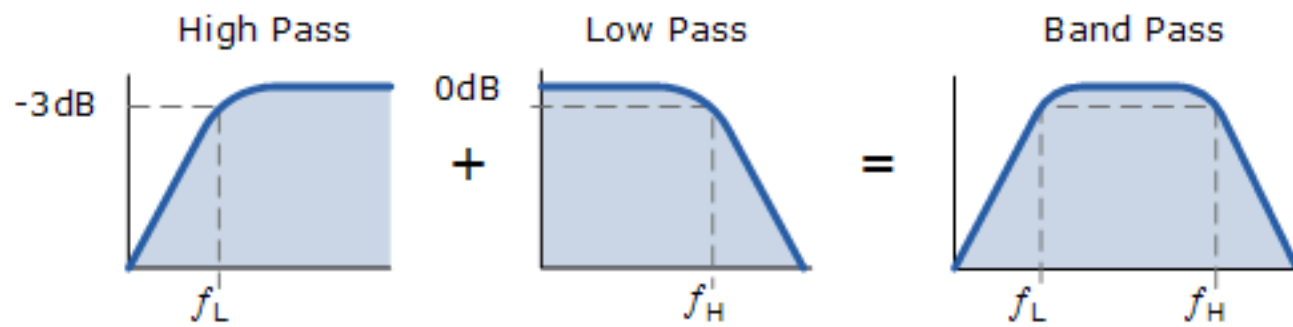
*Implies we need **TWO** different types of frequency-dependent circuit elements to design such filters*



Frequency-domain characteristics of *series connected L and C*

for both zero & infinity

Series connected

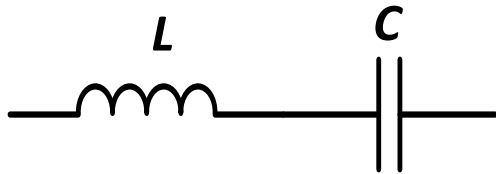

$$\omega = 0$$


$$\omega = \infty$$

$$|Z_{\text{series}}(j\omega)| \xrightarrow{\text{Block}} \infty$$

Frequency-domain impedance


$$Z_{\text{series}}(j\omega) = \underbrace{j\omega L}_{Z_L} + \underbrace{\frac{1}{j\omega C}}_{Z_C}$$
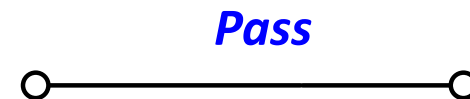
$$Z_{\text{series}}(j\omega_0) = 0 \quad \Rightarrow \quad \omega_0 = \sqrt{\frac{1}{LC}}$$



Frequency-domain characteristics of *parallel connected L and C*

Parallel connected

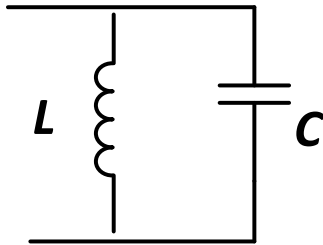

$$\omega = 0$$

$$\omega = \infty$$

$$\left| Z_{parallel}(j\omega) \right| \rightarrow \infty$$

Frequency-domain admittance

$$Z_{parallel}(j\omega_0) \rightarrow 0$$

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

$$Y_{parallel}(j\omega) = \frac{1}{j\omega L} + j\omega C$$


$Y_L \qquad Y_C$

Block




Band-Pass Filters




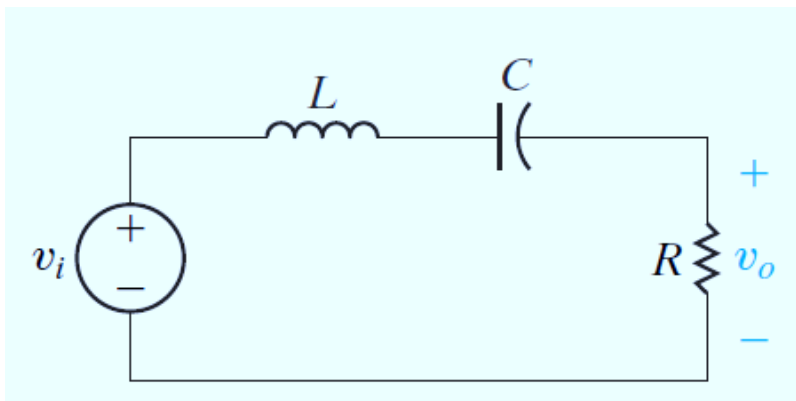
Are those who pass voltages within a band of frequencies to the output while filtering out voltages at frequencies outside this band



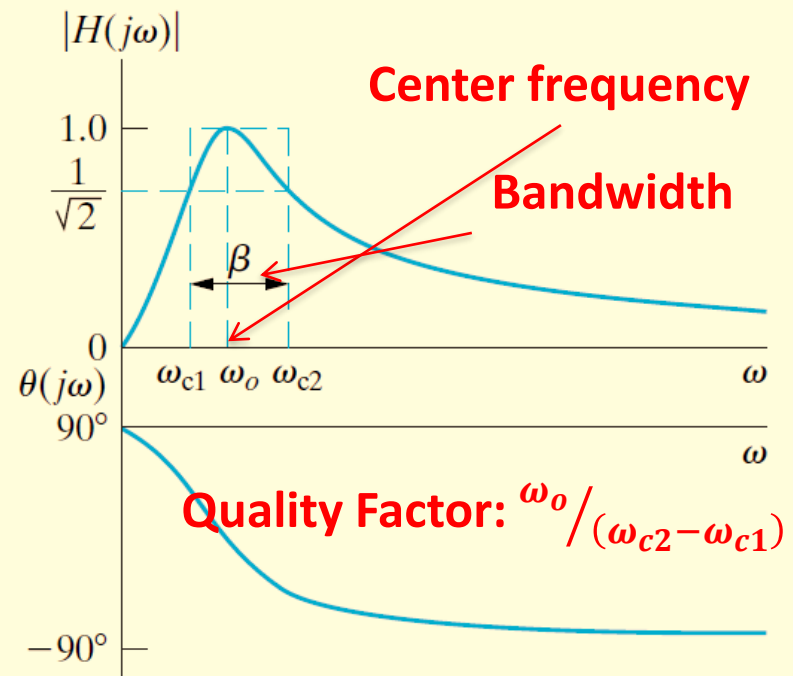
Cutoff frequencies are defined as the ones for which the magnitude of the transfer function equals $\frac{1}{\sqrt{2}} H_{max}$



Series RLC Circuit

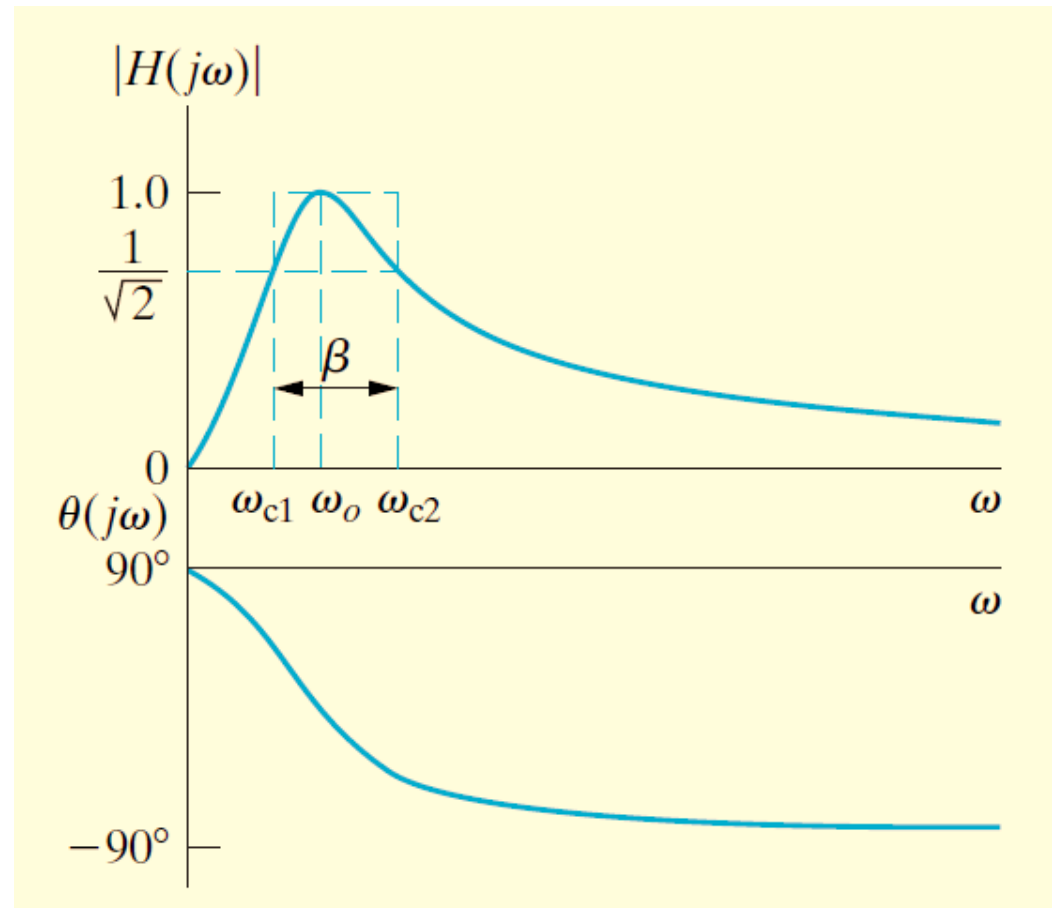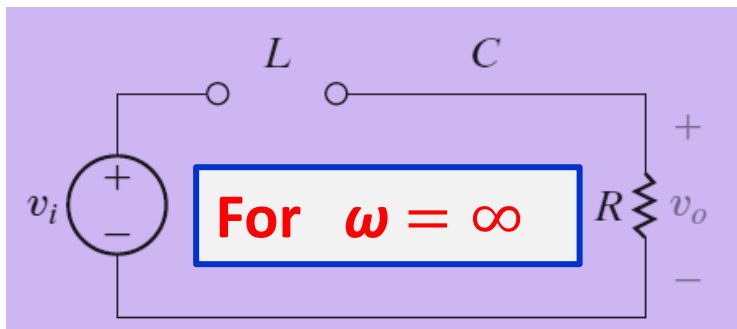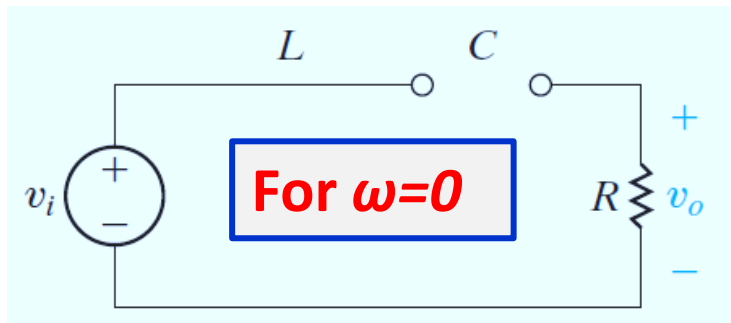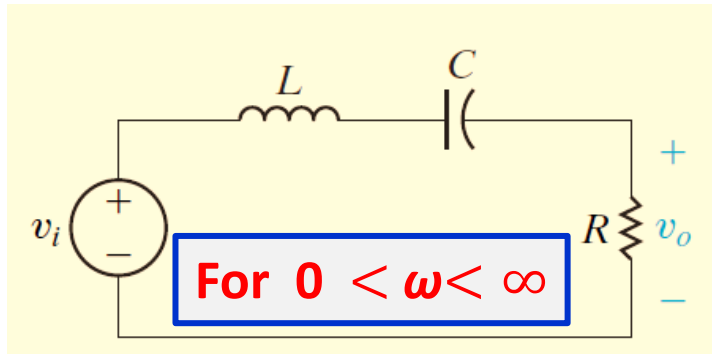

$$0 < \omega < \infty$$

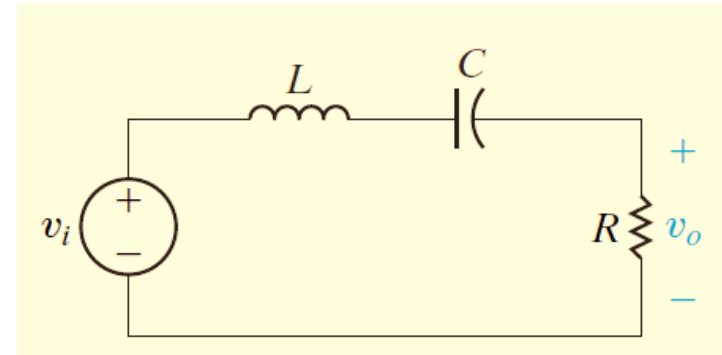

Between these two extremes, the capacitor C and the inductor L have finite impedances.


- Voltage supplied by the source drops across L and C and some voltage will reach the resistor.
- Z_C is negative, Z_L is positive: at some frequency, they are equal and opposite and cancel out: output voltage = source voltage.

$$Z_{series}(j\omega) = \underbrace{j\omega L}_{Z_L} + \underbrace{\frac{1}{j\omega C}}_{Z_C}$$

This special frequency is the center frequency

The series combination of L and C appears as a short circuit.

Transfer Function

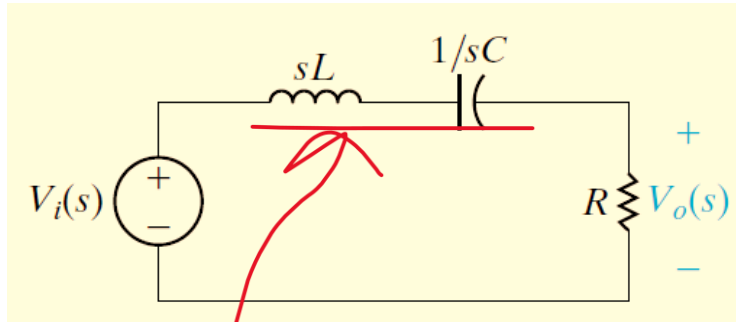

$$j\omega_o L + \frac{1}{j\omega_o C} = 0.$$

$$\omega_o = \sqrt{\frac{1}{LC}}.$$

$$H(s) = \frac{(R/L)s}{s^2 + (R/L)s + (1/LC)}.$$

$$|H(j\omega)| = \frac{\omega(R/L)}{\sqrt{[(1/LC) - \omega^2]^2 + [\omega(R/L)]^2}},$$

$$\theta(j\omega) = 90^\circ - \tan^{-1} \left[\frac{\omega(R/L)}{(1/LC) - \omega^2} \right].$$

The center frequency is defined as the frequency where the transfer function is purely real

Cutoff Frequencies ω_{c1} and ω_{c2}

$$H_{\max} = |H(j\omega_o)|$$

At center frequency H is maximum

$$\begin{aligned} &= \frac{\omega_o(R/L)}{\sqrt{[(1/LC) - \omega_o^2]^2 + (\omega_o R/L)^2}} \\ &= \frac{\sqrt{(1/LC)}(R/L)}{\sqrt{[(1/LC) - (1/LC)]^2 + [\sqrt{(1/LC)}(R/L)]^2}} = 1. \end{aligned}$$

Cutoff frequencies are defined as the ones for which the magnitude of the transfer function equals $1/\sqrt{2} H_{\max}$

$$\frac{1}{\sqrt{2}} = \frac{\omega_c(R/L)}{\sqrt{[(1/LC) - \omega_c^2]^2 + (\omega_c R/L)^2}} = \frac{1}{\sqrt{[(\omega_c L/R) - (1/\omega_c RC)]^2 + 1}}.$$

Cutoff frequencies ω_{c1}, ω_{c2}

$$\pm 1 = \omega_c \frac{L}{R} - \frac{1}{\omega_c RC}.$$

$$\omega_c^2 L \pm \omega_c R - 1/C = 0.$$

$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)},$$

$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}.$$

The two positive values of the second order equation have physical meaning and identify the passband of the filter

Center Frequency ω_o

$$\omega_o = \sqrt{\omega_{c1} \cdot \omega_{c2}}$$

The center frequency is the geometric mean of the two cutoff frequencies

$$= \sqrt{\left[-\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)} \right] \left[\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)} \right]}$$

$$= \sqrt{\frac{1}{LC}}$$

Bandwidth

$$\beta = \omega_{c2} - \omega_{c1}$$

$$= \left[\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)} \right] - \left[-\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)} \right]$$

$$= \frac{R}{L}.$$


Cutoff frequencies in terms of the center frequencies and bandwidth




$$\omega_{c1} = -\frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_o^2},$$

$$\omega_{c2} = \frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_o^2}.$$

Q Factor

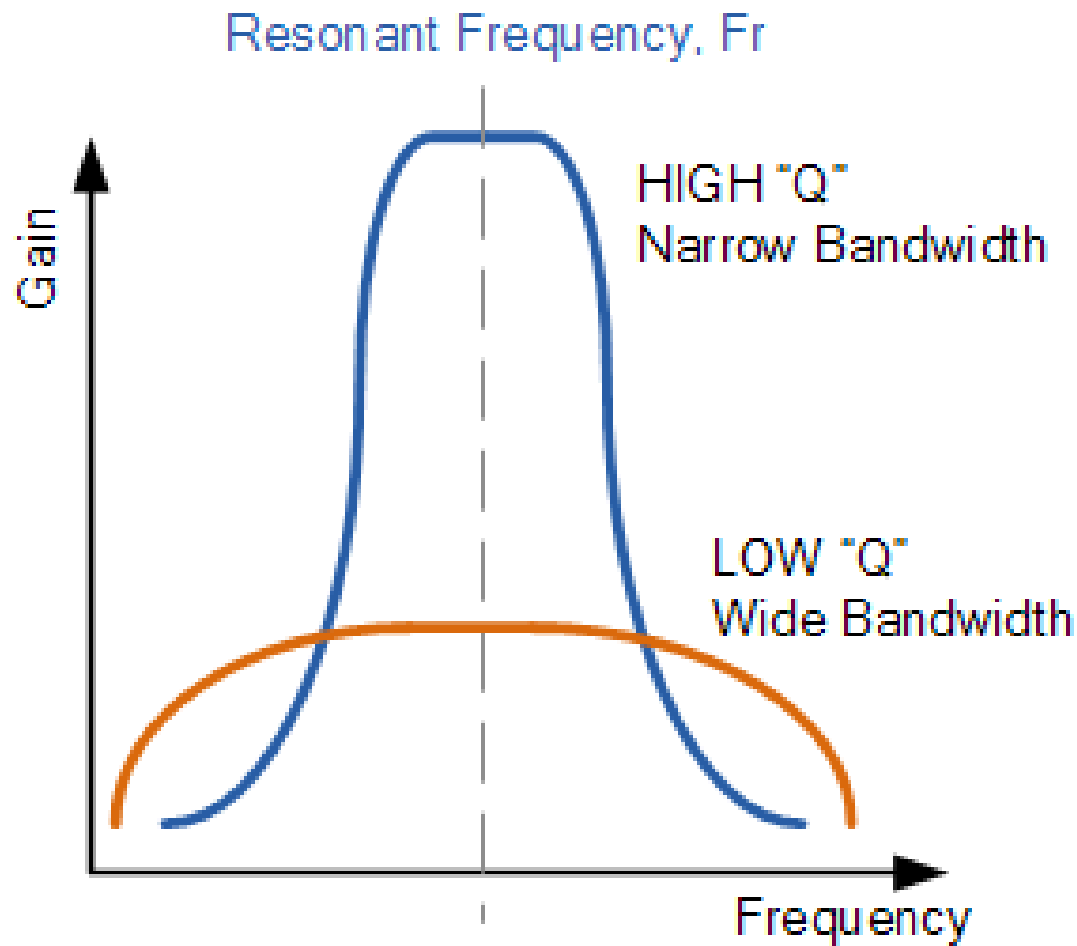


RLC Bandpass Filter

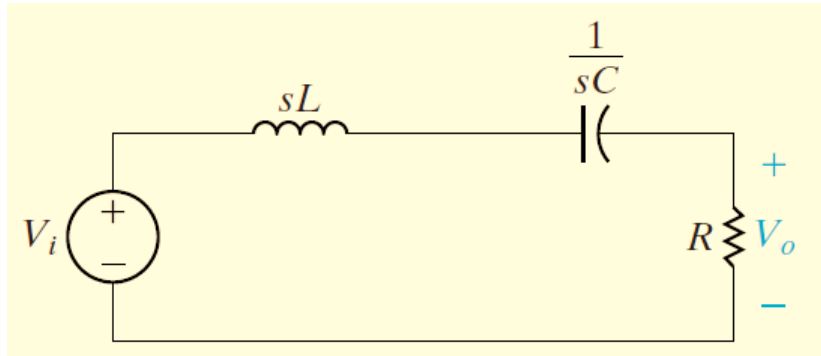

$$H(s) = \frac{(R/L)s}{s^2 + (R/L)s + 1/LC}$$

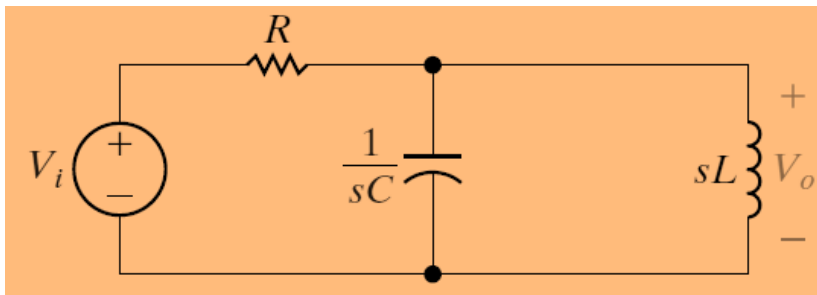
$$\omega_o = \sqrt{1/LC} \quad \beta = R/L$$



$$H(s) = \frac{s/RC}{s^2 + s/RC + 1/LC}$$


$$\omega_o = \sqrt{1/LC} \quad \beta = 1/RC$$

Effect of non ideal voltage source

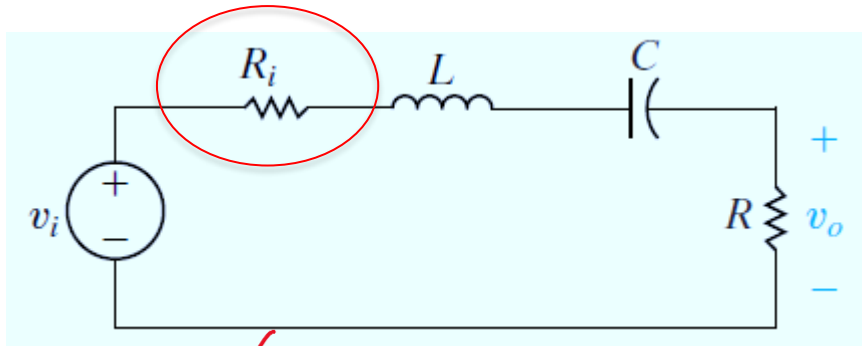


$$H(s) = \frac{\beta s}{s^2 + \beta s + \omega_o^2}$$

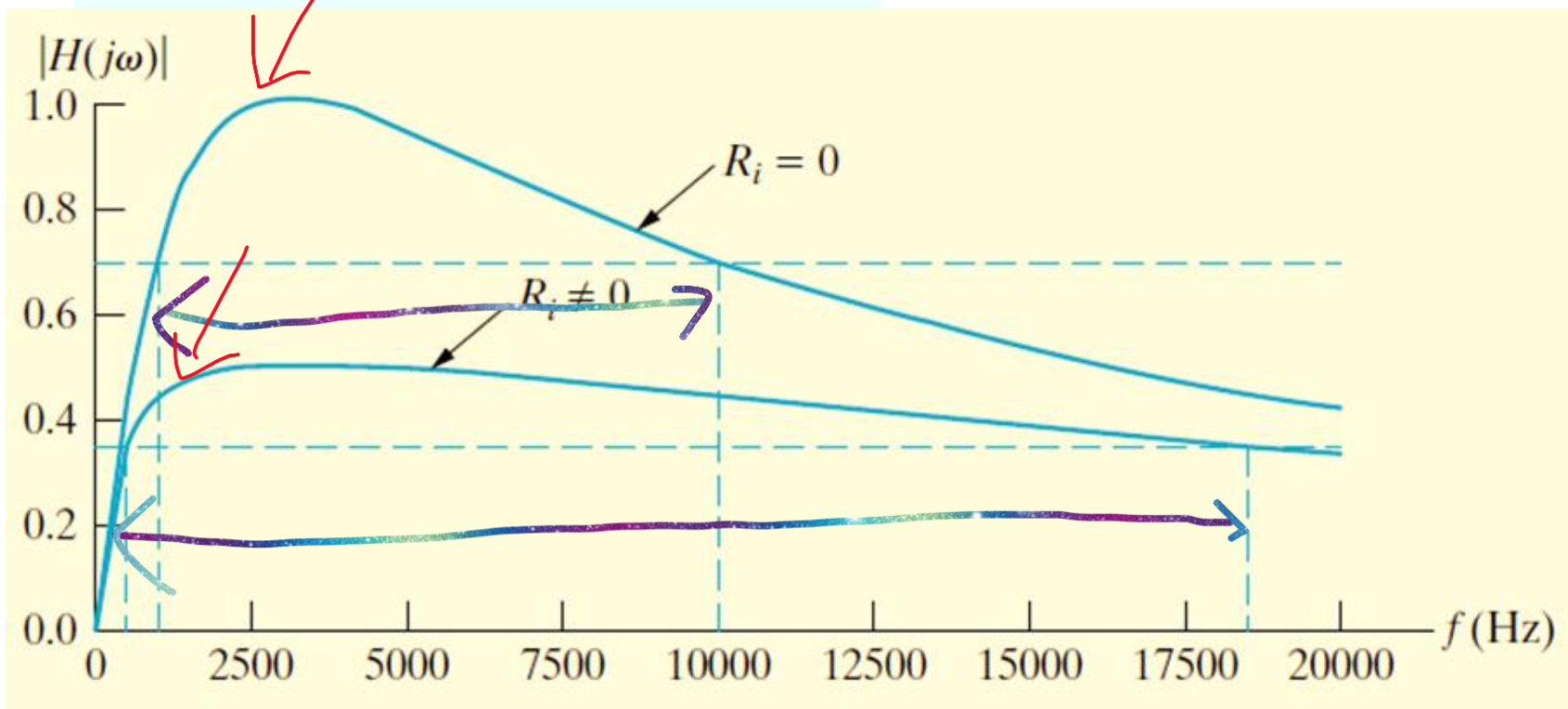The transfer function $H(s)$ is shown with the terms βs in the numerator and βs in the denominator circled in red.



Effect of non ideal voltage source

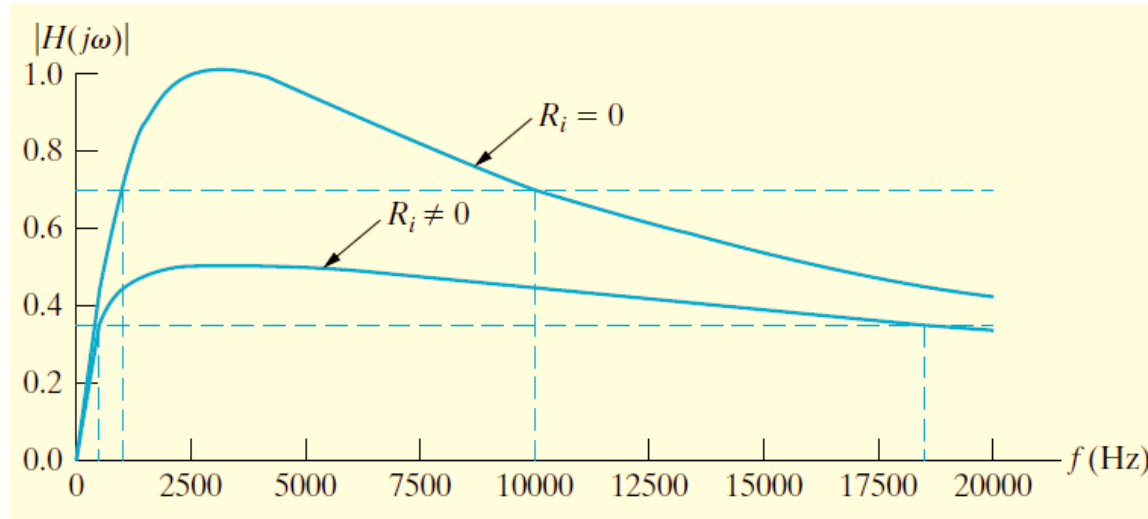

- The maximum transfer function magnitude for the filter with $R_i \neq 0$ is smaller than for the filter with $R_i = 0$
- The bandwidth for the filter with $R_i \neq 0$ is larger than that for the filter with $R_i = 0$
- The cutoff frequencies for the two circuits are also different.

Transfer Function


$$H(s) = \frac{\beta s}{s^2 + \beta s + \omega_o^2}.$$


Effect of non ideal voltage source

$$H(s) = \frac{K \beta s}{s^2 + \beta s + \omega_o^2},$$

Where K and β depend on whether the series resistance of the voltage source is zero or non zero

Examples

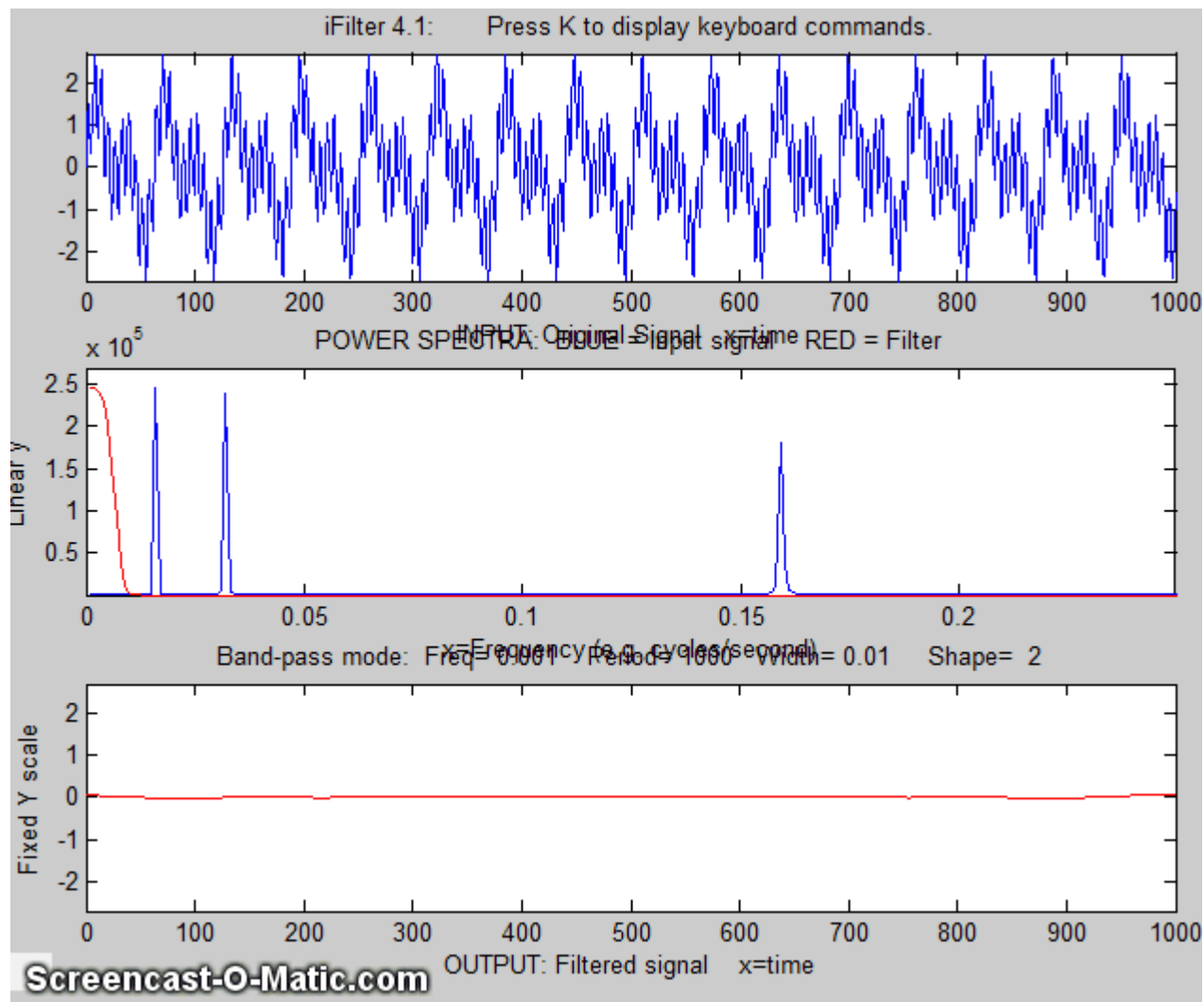


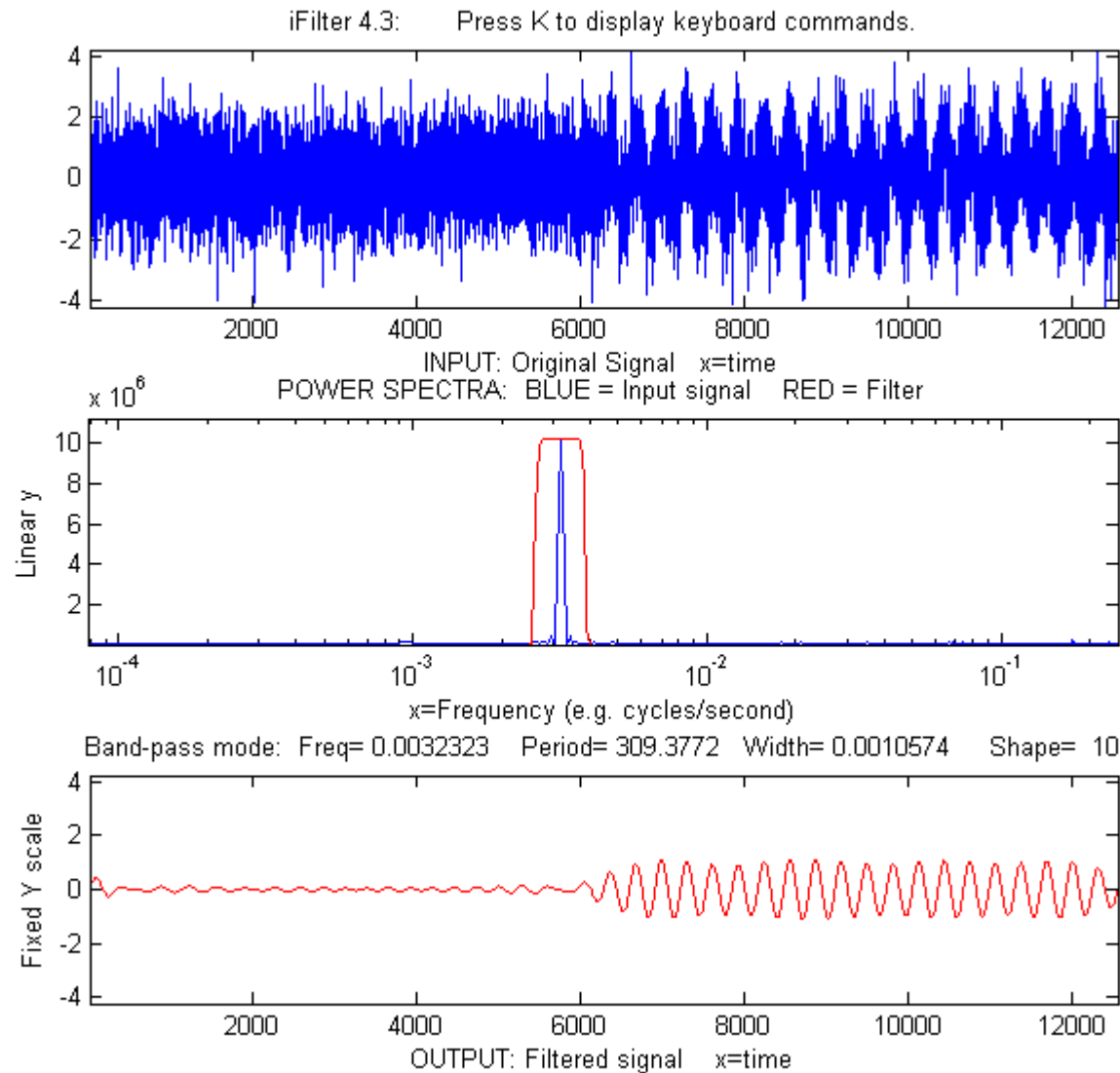


Band-reject filter

Band-Reject Filters

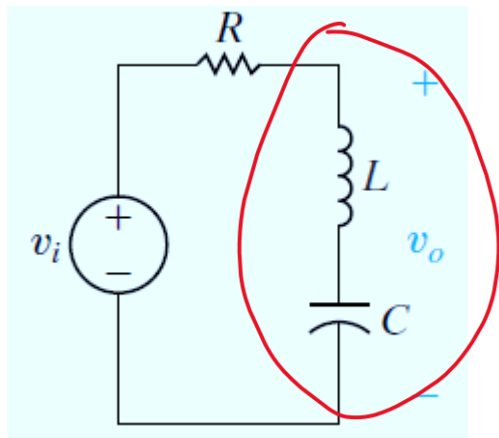
Are those which pass source voltages outside the band between the two cutoff frequencies to the output and attenuates source voltages between the two cutoff frequencies



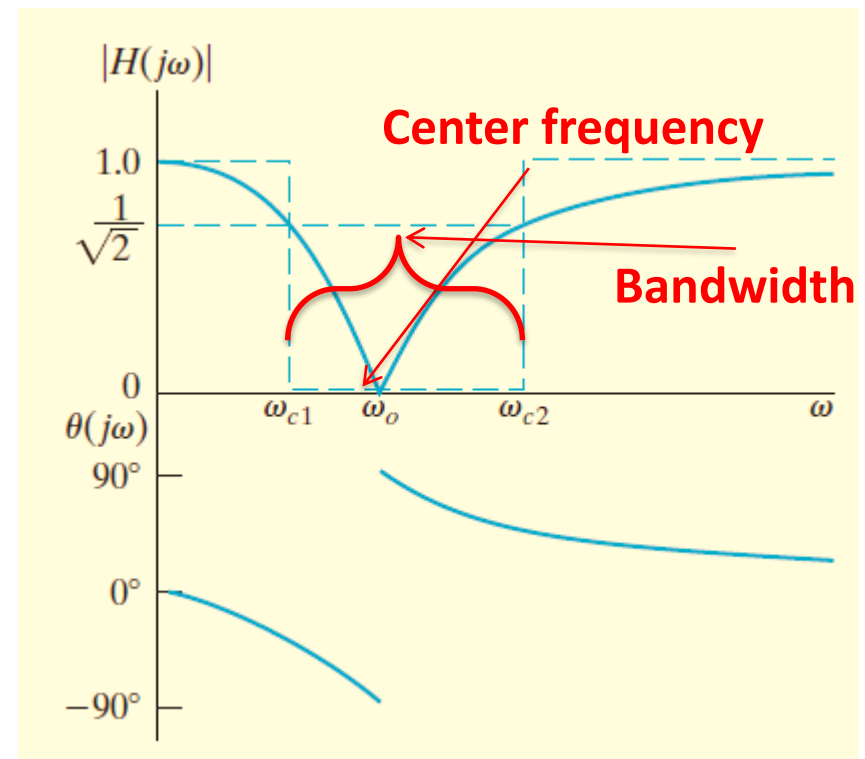
The output voltage is now defined accross the inductor-capacitor pair




Bandreject Filters

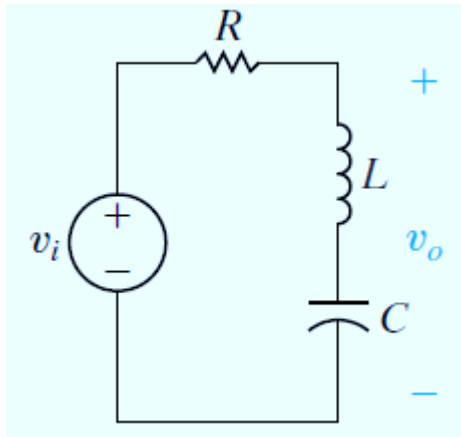

For $0 < \omega < \infty$


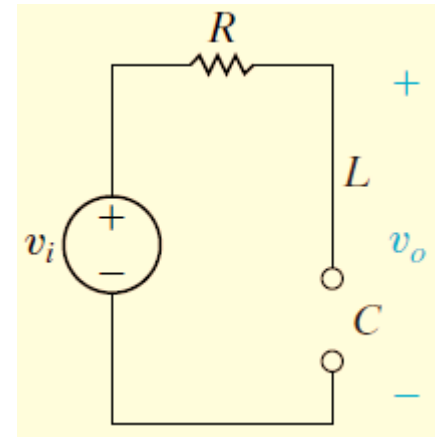


For $\omega = 0$

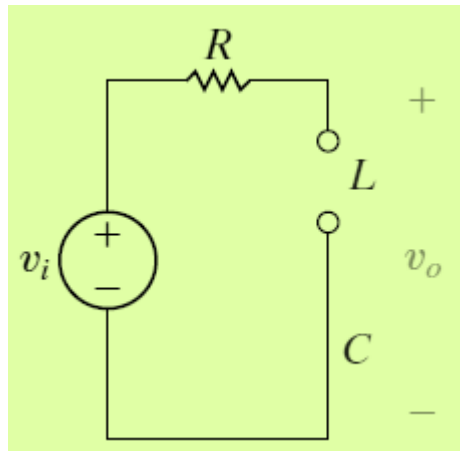

For $\omega = \infty$

Series RLC Circuit

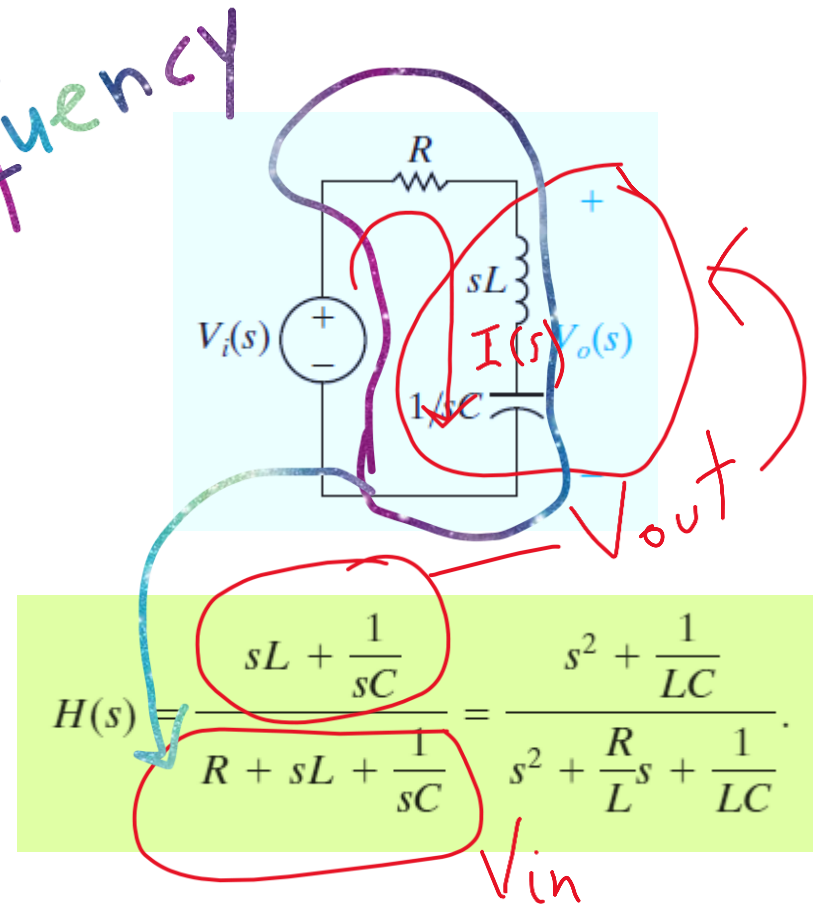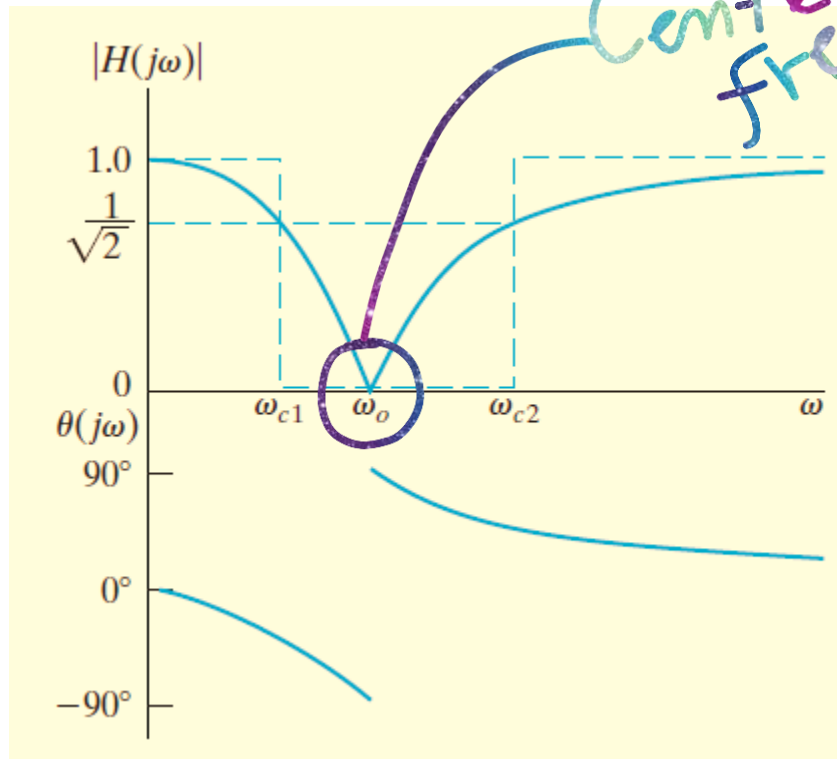

Between the two passbands, inductor and capacitor have finite impedances of opposite signs.

$$Z_{series}(j\omega) = \underbrace{j\omega L}_{Z_L} + \underbrace{\frac{1}{j\omega C}}_{Z_C}$$

As frequency increases from zero, the impedance of the inductor increases and that of the capacitor decreases

Center Frequency ω_o

$$\omega_o = \sqrt{\frac{1}{LC}}.$$

$$H_{\max} = |H(j0)| = |H(j\infty)|,$$

The center frequency is the frequency for which the sum of the impedances of the capacitor and inductor is zero

$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}},$$

$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}.$$

$$Z_{\text{series}}(j\omega) = \underbrace{j\omega L}_{Z_L} + \frac{1}{\underbrace{j\omega C}_{Z_C}}$$

At some frequency between the two passbands, the impedances of the inductor and capacitor are equal but of opposite sign. At this frequency, the series combination of L and C is a short circuit: output voltage is zero. This is the center frequency of this series RLC bandreject filter.

Bode plot values: Magnitude & Phase

Handnote

$$|H(j\omega)| = \frac{\left| \frac{1}{LC} - \omega^2 \right|}{\sqrt{\left(\frac{1}{LC} - \omega^2 \right)^2 + \left(\frac{\omega R}{L} \right)^2}},$$

$$\omega_o = \sqrt{\frac{1}{LC}}.$$

$$\theta(j\omega) = -\tan^{-1}\left(\frac{\frac{\omega R}{L}}{\frac{1}{LC} - \omega^2}\right).$$

The phase shift between the input and the output approaches **-90°** as **ωL** approaches **$1/\omega C$** . As soon as **ωL** exceeds **$1/\omega C$** the phase shift jumps to **+90°** and then approaches zero as **ω** continues to increase.


Loaded & non-ideal sources filters




Load: Adding a load to the output of a passive filter changes its filtering properties by altering the location and magnitude of the passband.

Non-ideal sources: Replacing an ideal voltage source with one whose source resistance is nonzero also changes the filtering properties of the rest of the circuit, again by altering the location and magnitude of the passband.

Audio & Radio Frequencies

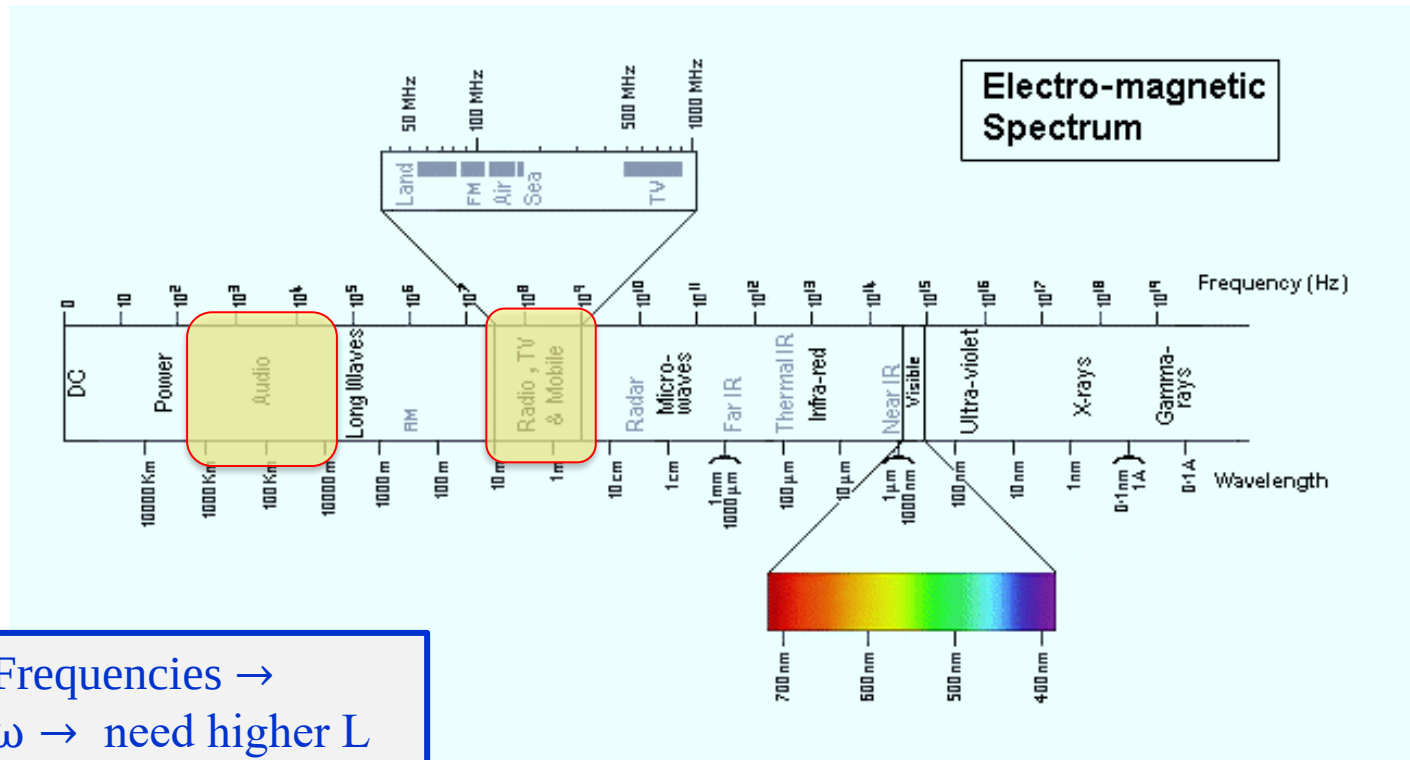

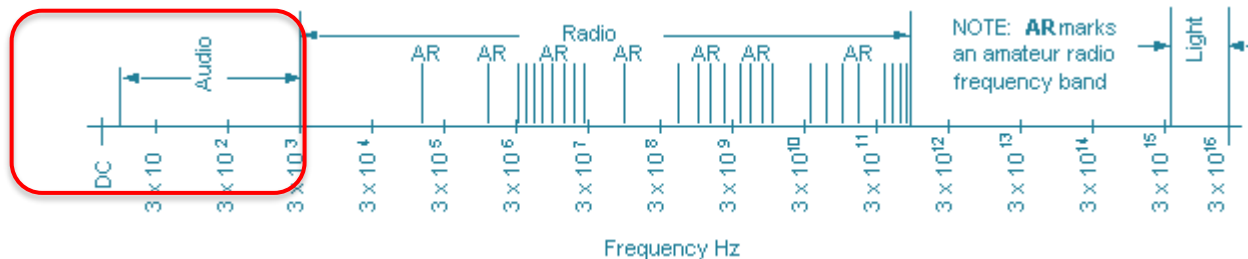Audio Frequencies →
lower ω → need higher L



Passive Filters: Review

- Made up of passive components - resistors, capacitors and inductors
- No amplifying elements (transistors, op-amps, etc)
- No signal gain
- Require no power supplies
- Desirable to use inductors with high quality factors $\left[Q = \frac{\omega L}{R} \right]$

$$X_L = \omega L$$



Audio Frequencies: bulky inductors
Radio Frequencies: OK

End