

TTK4240 Industriell elektroteknikk

January 21, 2025

Marta Molinas

Institutt for teknisk kybernetikk

Lecture - Week 04 Part II

- Review of the fundamentals in circuit analysis with sinusoidal signals
 - The concept of Phasor
- Current, voltage and power calculations
 - Instantaneous power
 - Average (real) power
 - Reactive power
 - Complex power
 - Power factor
 - Maximum real power delivered to a load
 - Load impedance required to deliver maximum real power to the load

Review and practical examples for Chapter 9 and 10

Phasor and property

Definition


- Phasor is complex number defined at a specific frequency being used for representing a sinusoid.

$$\underline{Ae^{j\theta}} \text{ at } \omega \longleftrightarrow A \cos(\omega t + \theta)$$

Property

$$\underbrace{Ae^{j\theta}}_{\text{at } \omega} \rightarrow H(s) \rightarrow \underbrace{H(j\omega)}_{\text{at } \omega} \cdot Ae^{j\theta}$$

Active and reactive power

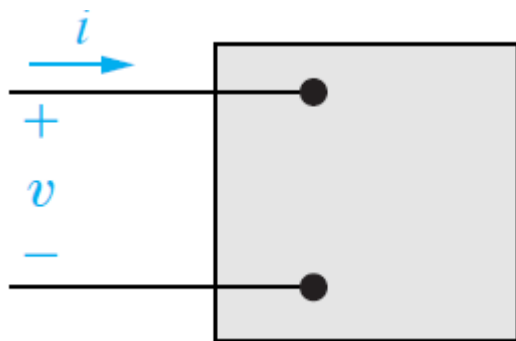

$$v = V_m \cos(\omega t + \theta_v),$$

$$i = I_m \cos(\omega t + \theta_i),$$

Instantaneous power is defined as $p = vi$.

$$p = P + P \cos 2\omega t - Q \sin 2\omega t,$$

Active power

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i),$$

Reactive power


$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i).$$

Apparent power


$$\left. \begin{aligned} P &= \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \\ Q &= \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \end{aligned} \right\}$$

$$\sqrt{P^2 + Q^2} = \frac{V_m I_m}{2} = S$$


Apparent power

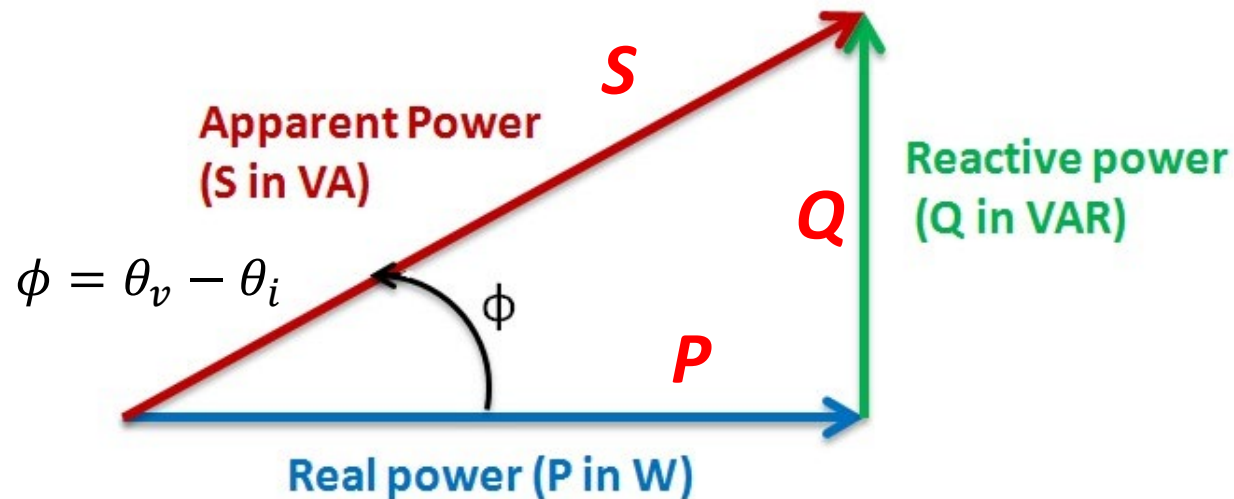

Power factor

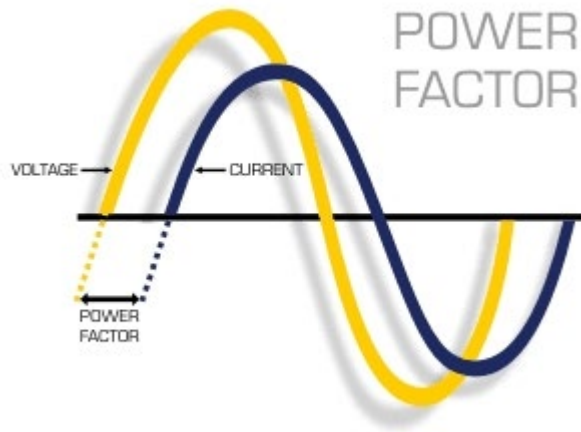

Voltage phasor U

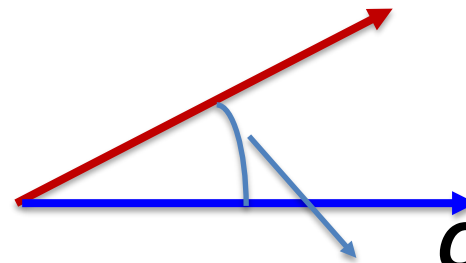

Current phasor I


Angle difference $\theta_v - \theta_i$



Power factor

$$\text{pf} = \cos(\theta_v - \theta_i),$$


Power factor

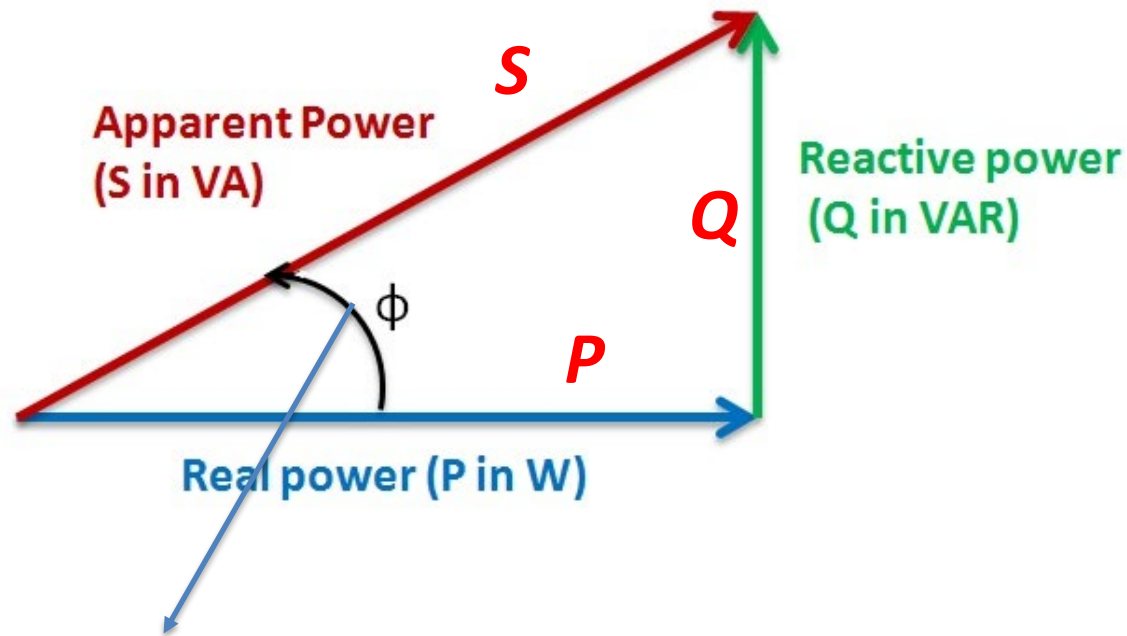


$$\cos(\theta_v - \theta_i) = \cos \phi = \frac{P}{S}$$

Leading and lagging PF

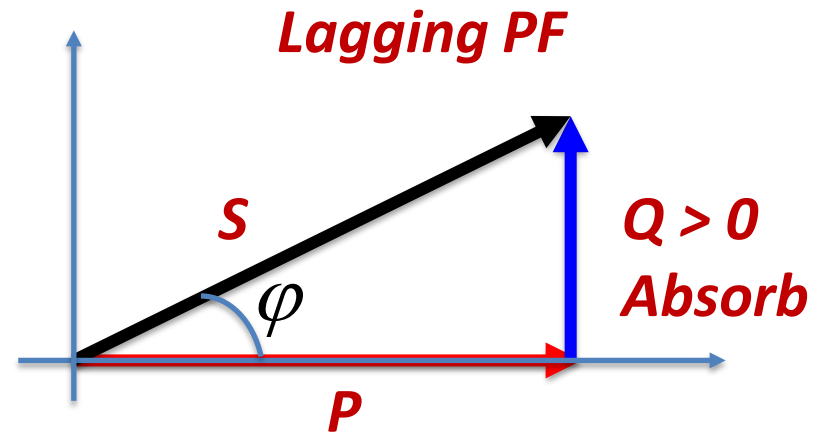The **lagging PF** refers to the current flowing through the circuit will be **lagging** the voltage (i.e. **$Q > 0$**)




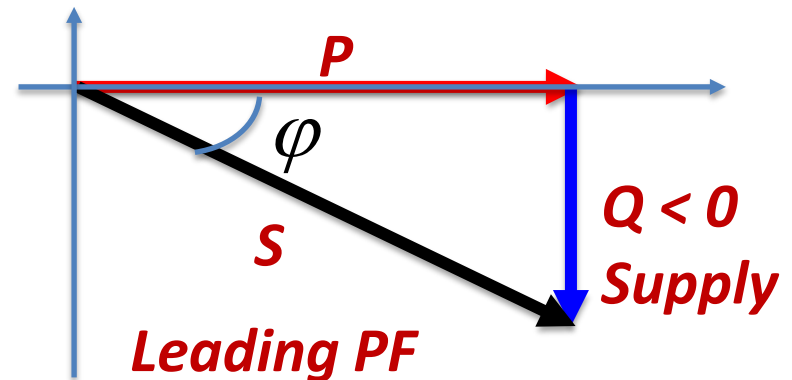The **leading PF** refers to the current flowing through the circuit will be **leading** the voltage (i.e. **$Q < 0$**)



Practical Example of Application

Calculate Average and Reactive Power

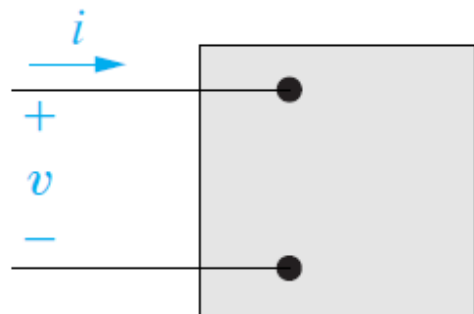

$$v = 100 \cos(\omega t + 15^\circ) \text{ V},$$

$$i = 4 \sin(\omega t - 15^\circ) \text{ A}.$$

- a) Calculate the average power and the reactive power
- b) Is the network absorbing or delivering power?
- c) Is the network inside the box absorbing or supplying reactive power?


Question a) Calculate the average power and the reactive power ?

$$v = 100 \cos(\omega t + 15^\circ)$$

$$i = 4 \sin(\omega t - 15^\circ)$$

$$i = 4 \cos(\omega t - 15^\circ - 90^\circ)$$

$$v = 100 \cos(\omega t + 15^\circ)$$

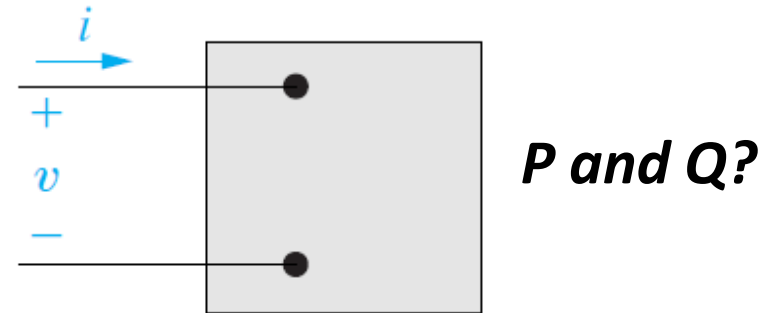

$$\theta_i = -105^\circ \quad \text{Current phase}$$

$$\theta_v = 15^\circ \quad \text{Voltage phase}$$

$$V_m = 100$$

$$I_m = 4$$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i),$$

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i).$$

Question a) Calculate the average power and the reactive power ?

Active power

$$P = \frac{4 * 100}{2} \cos(15^\circ - (-105^\circ))$$
$$= 200 \cos(120^\circ) = -100$$

$$\theta_i = -105^\circ$$

$$\theta_v = 15^\circ$$

$$V_m = 100$$

$$I_m = 4$$

Reactive power

$$Q = \frac{4 * 100}{2} \sin(15^\circ - (-105^\circ))$$
$$= 200 \sin(120^\circ) = 100\sqrt{3}$$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i),$$

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i).$$

A check

$$\sqrt{P^2 + Q^2} = S$$

$$S = \frac{100 \cdot 4}{2} = 200$$

$$\sqrt{P^2 + Q^2} = \sqrt{(-100)^2 + (100\sqrt{3})^2} = 200$$

$$\theta_i = -105^\circ$$

$$\theta_v = 15^\circ$$

$$V_m = 100$$

$$I_m = 4$$


Question b) and c)

b) Is the network absorbing or delivering power?

Delivering

c) Is the network inside the box absorbing or supplying reactive power (magnetizing vars)?

Absorbing

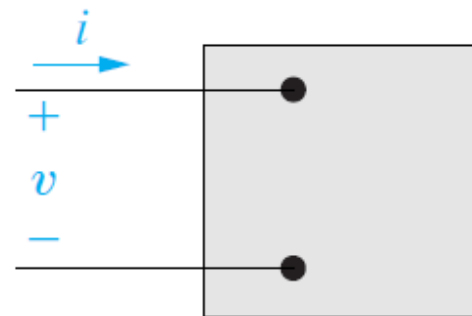

$$P = -100$$

$$Q = 100\sqrt{3}$$


What is the PF?

$$\theta_i = -105^\circ, \theta_v = 15^\circ$$

$$\cos(\theta_v - \theta_i)$$


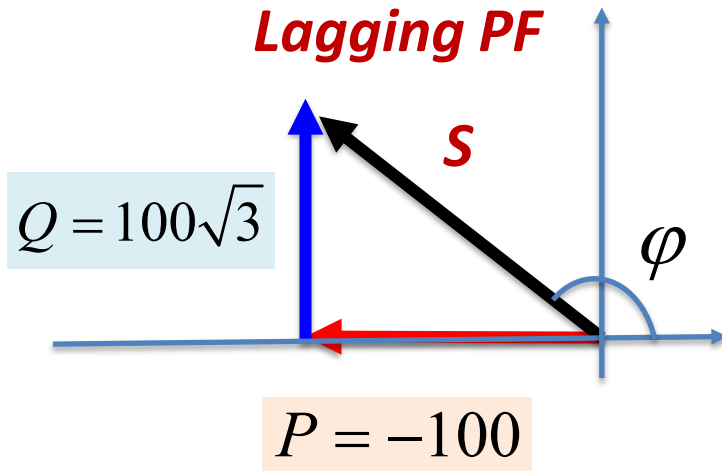
$$= \cos\left(15 - (-105^\circ)\right) = \cos(120^\circ) = -\frac{1}{2}$$




$$\cos(\varphi) = \frac{P}{S} = \frac{-100}{200} = \boxed{-}\frac{1}{2}$$

The negative sign indicates the active power is inversed (delivery)

Review of the RMS value calculation

RMS Value and Power calculations


AC system

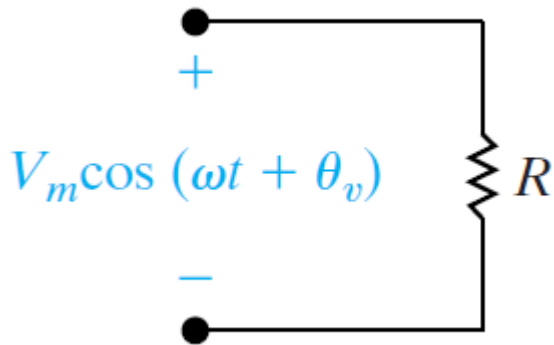

$$P = \frac{1}{T} \int_{t_0}^{t_0+T} \frac{V_m^2 \cos^2(\omega t + \phi_v)}{R} dt$$

$$= \frac{1}{R} \left[\underbrace{\frac{1}{T} \int_{t_0}^{t_0+T} V_m^2 \cos^2(\omega t + \phi_v) dt}_{V_{rms}^2} \right]$$


DC system

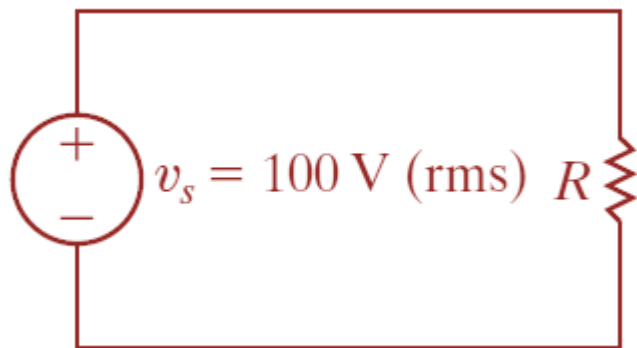

←
Equivalent

$$P = \frac{V_{rms}^2}{R}$$

RMS Value and Power calculations

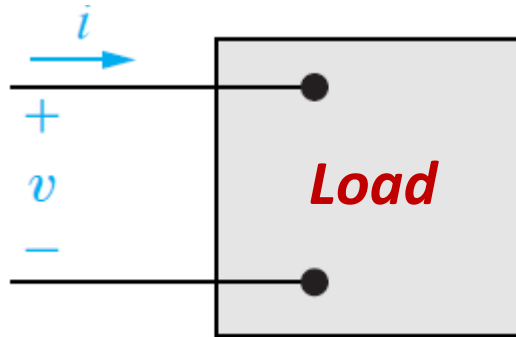

$$v = V_m \cos(\omega t + \theta_v)$$

$$i = I_m \cos(\omega t + \theta_i)$$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i),$$

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i).$$

$\theta_v = \theta_i$ Is the case with a pure resistive load

$\theta_v \neq \theta_i$ Some capacitors or inductors exist in the system

Effective Value of Power

Effective value of active power

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i)$$

$$= V_{eff} I_{eff} \cos(\theta_v - \theta_i)$$


Effective value of reactive power

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$$

$$= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \sin(\theta_v - \theta_i)$$



$$= V_{eff} I_{eff} \sin(\theta_v - \theta_i)$$

Equivalent DC systems

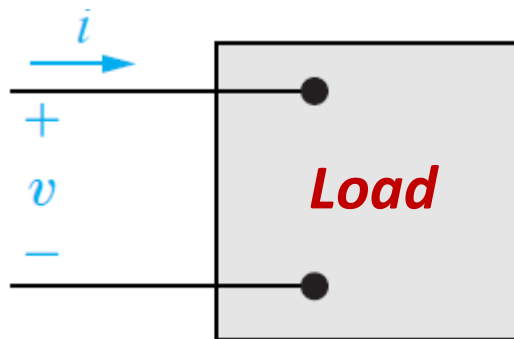

$$v = V_m \cos(\omega t + \theta_v)$$

$$i = I_m \cos(\omega t + \theta_i)$$

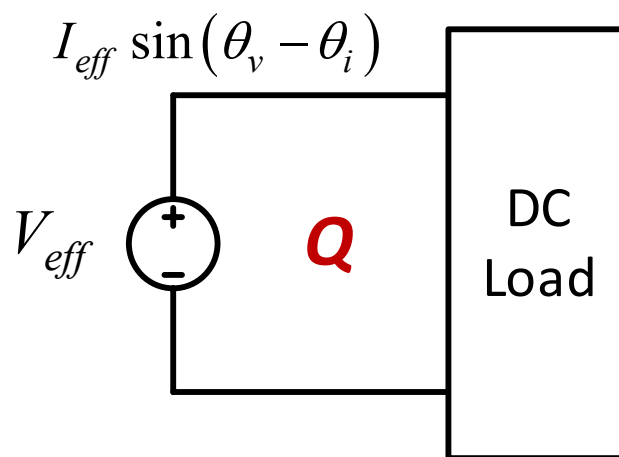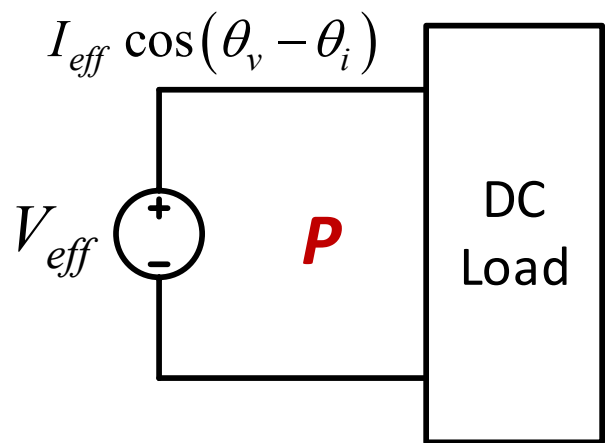


Reactive Power

$$Q = V_{\text{eff}} I_{\text{eff}} \sin (\theta_v - \theta_i).$$

- The rating of equipments depends on Q
- The magnetic and electric fields of inductors and capacitors store energy related to Q

Complex Power

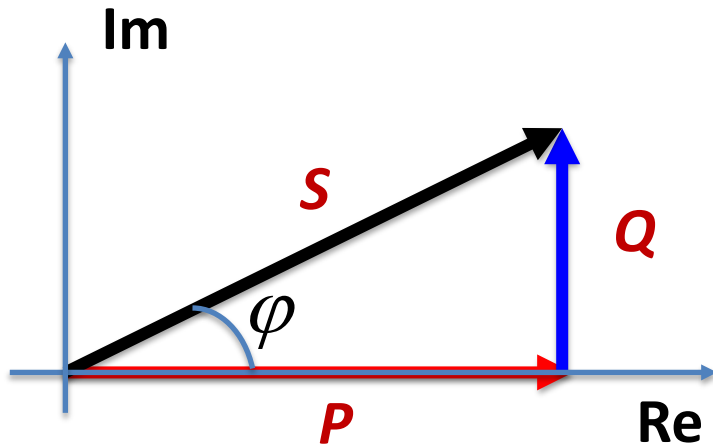

Complex power

$$S = P + jQ$$

$$P = V_{eff} I_{eff} \cos(\theta_v - \theta_i)$$

$$Q = V_{eff} I_{eff} \sin(\theta_v - \theta_i)$$

$$S = V_{eff} I_{eff} (\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i))$$

Complex power and phasors

$$S = V_{eff} I_{eff} \left(\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i) \right)$$



Applying Euler identity

$$S = V_{eff} I_{eff} e^{j(\theta_v - \theta_i)}$$

$$= \left[V_{eff} e^{j\theta_v} \right] \cdot \left[I_{eff} e^{-j\theta_i} \right]$$

Voltage phasor **V**

Conjugate of current phasor **I**




Complex power represented by voltage and current phasors

$$S = V_{eff} \cdot I_{eff}^*$$

$$S = \frac{1}{2} V_m \cdot I_m^*$$

Complex power with Impedances

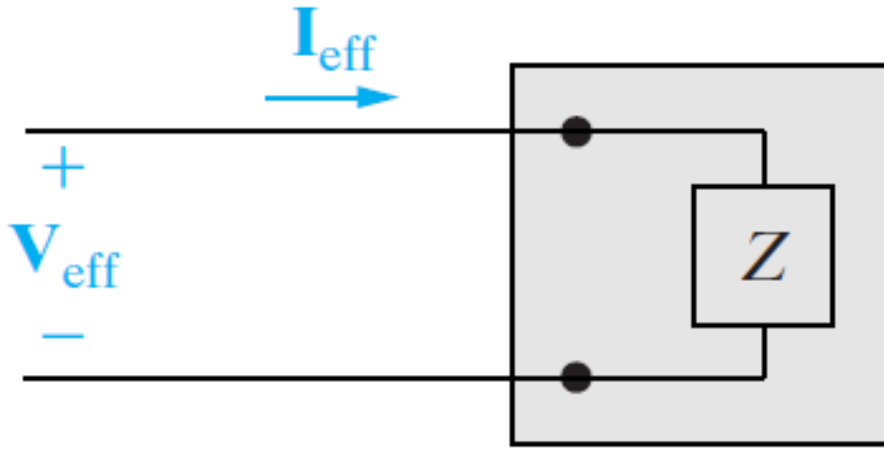

$$S = V_{eff} I_{eff}^*$$

$$V_{eff} = Z I_{eff}$$

Replace current
with voltage

$$S = V_{eff} \left(\frac{V_{eff}}{Z} \right)^* \Rightarrow S = \frac{|V_{eff}|^2}{Z^*}$$

Replace voltage
with current


$$S = Z I_{eff} I_{eff}^* \Rightarrow S = Z |I_{eff}|^2$$

Complex power of R, L, C

Resistor

$$Z = R$$

$$S = \frac{|V_{eff}|^2}{R} = P \quad P > 0$$

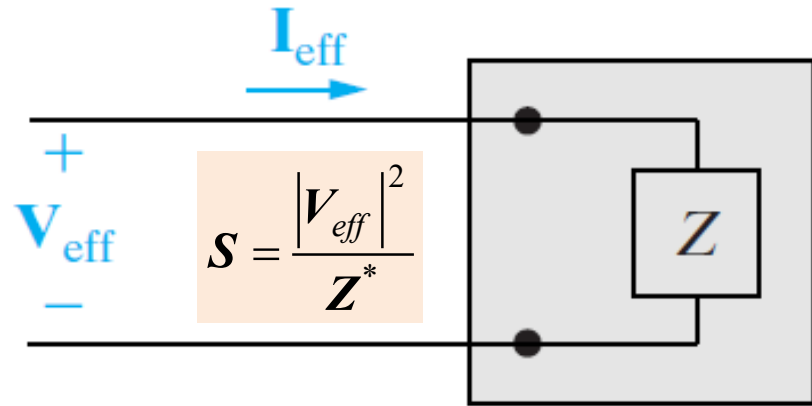

Inductor

$$Z = jX \quad (X > 0)$$

$$S = \frac{|V_{eff}|^2}{-jX} = j \frac{|V_{eff}|^2}{X} = jQ \quad Q > 0$$


Capacitor

$$Z = jX \quad (X < 0)$$

$$S = \frac{|V_{eff}|^2}{-jX} = j \frac{|V_{eff}|^2}{X} = jQ \quad Q < 0$$

Phasor diagram


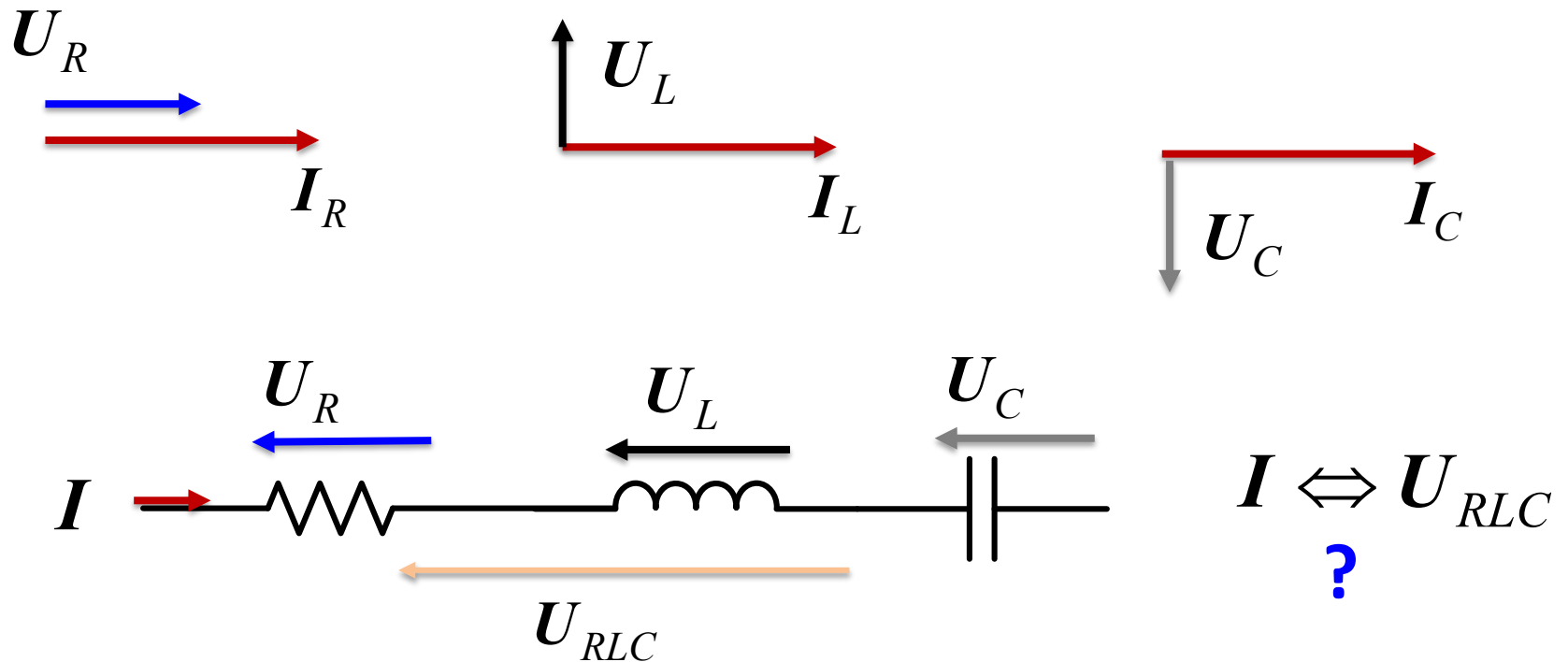
Phasor Diagram is a graphical way of representing the magnitude and directional relationship between two or more phasors.





Phasor diagram of a series connected RLC circuit

$$U_{RLC} = U_R + U_L + U_C$$

$$I = I_R = I_L = I_C$$

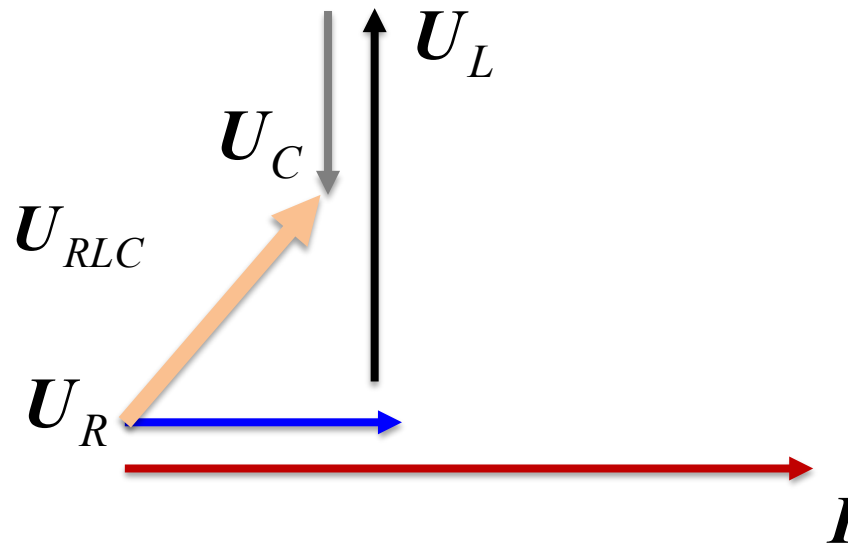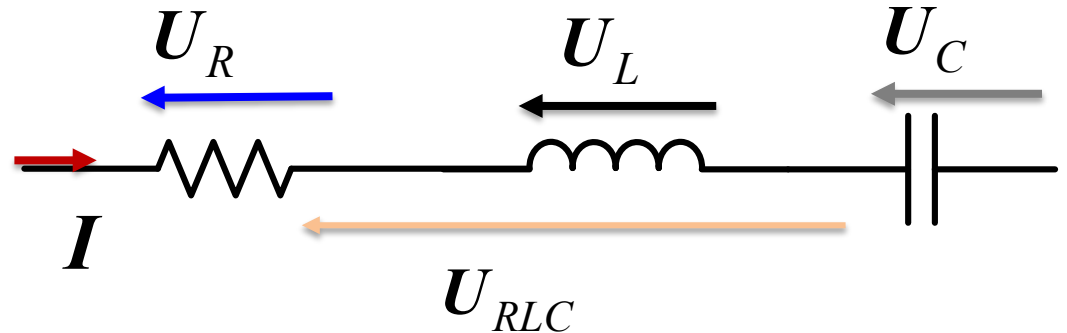

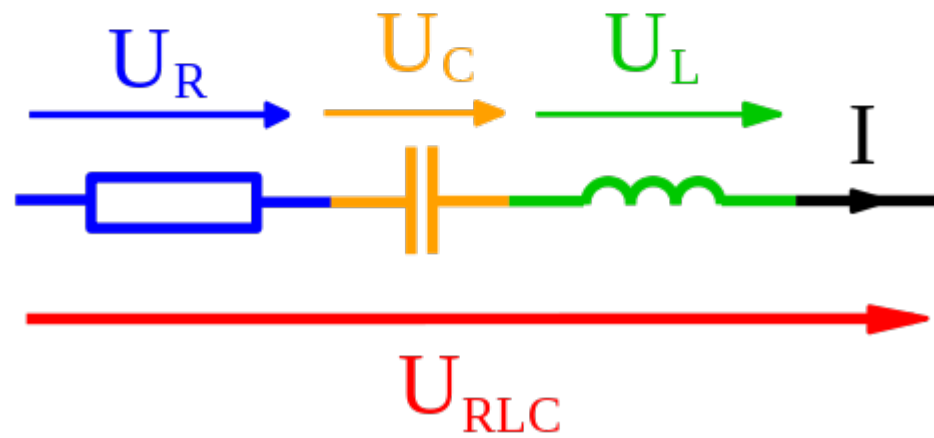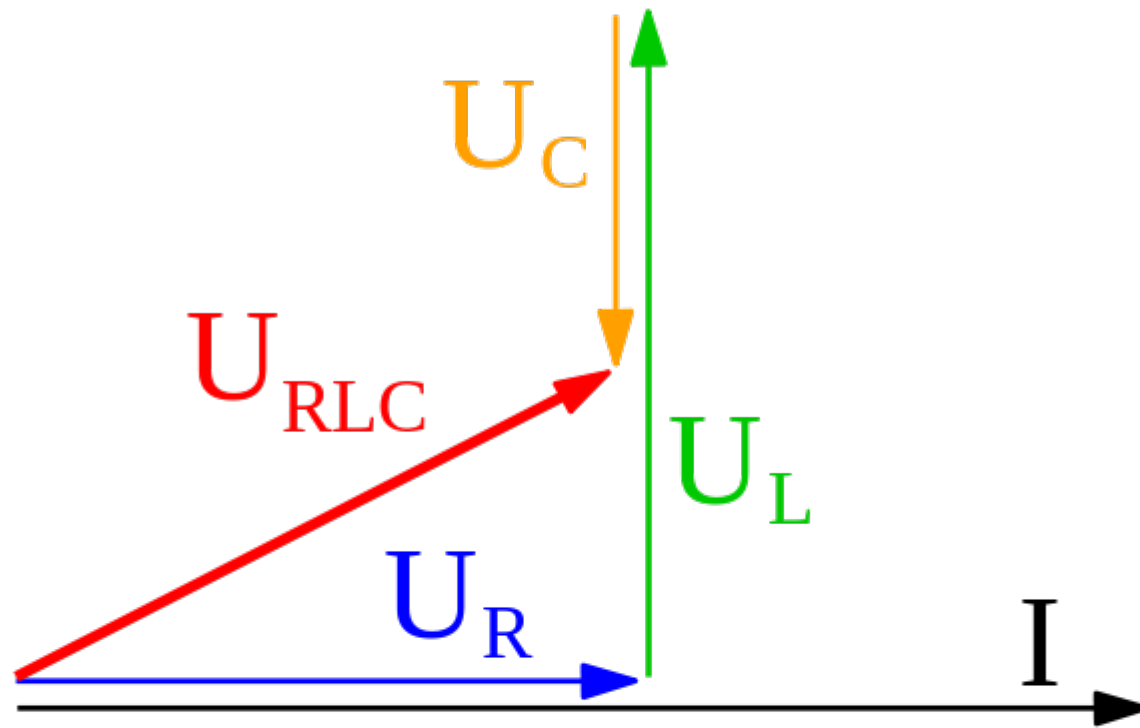

Practical Example of Application

Appliances consumption

Appliance	Average Wattage	Est. kWh Consumed Annually ^a
Food preparation		
Coffeemaker	1200	140
Dishwasher	1201	165
Egg cooker	516	14
Frying pan	1196	100
Mixer	127	2
Oven, microwave (only)	1450	190
Range, with oven	12,200	596
Toaster	1146	39

$$S = V_{eff} I_{eff}^*$$

$$P = V_{eff} I_{eff}$$

If the kitchen outlets (120 V) are protected by a 20A fuse, and assuming that the Coffee maker, egg cooker, frying pan and toaster are in operation at the same time:

Will the circuit be interrupted by the protecting device?

Calculation

The total power of Coffee maker, egg cooker, frying pan and toaster is

$$\begin{aligned} P &= \\ 1200 + 516 + 1196 + 1146 \\ &= 4058 \text{ W} \end{aligned}$$

$$|I_{eff}| = \left| \frac{S^*}{V_{eff}^*} \right| = \frac{P}{V_{eff}} = \frac{4058 \text{ W}}{120 \text{ V}} = 33.8 \text{ A} > 20 \text{ A}$$

Appliance	Average Wattage	Est. kWh Consumed Annually ^a
Food preparation		
Coffeemaker	1200	140
Dishwasher	1201	165
Egg cooker	516	14
Frying pan	1196	100
Mixer	127	2
Oven, microwave (only)	1450	190
Range, with oven	12,200	596
Toaster	1146	39

The circuit will be interrupted

Practical Example

Calculate Complex Power

An electrical load operates at 240 V rms, absorbing 8 kW at a lagging power factor of 0.8:


- a) Calculate the complex power of the load
- b) Calculate the impedance of the load

$$U_{eff} = 240V$$

$$P = 8kW$$

$$\cos \varphi = 0.8$$


$$\varphi > 0$$

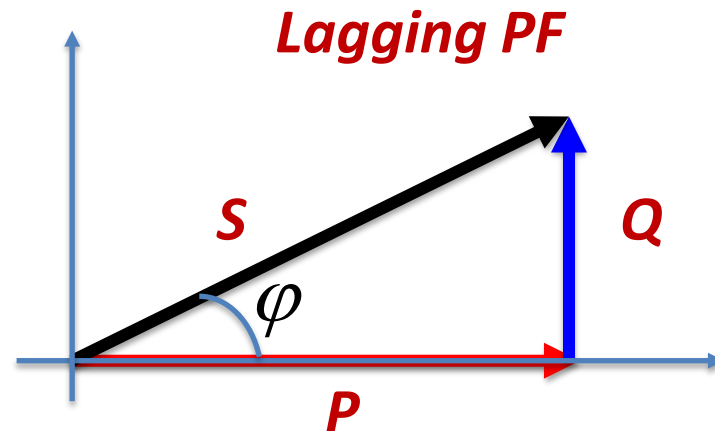

Calculate Complex Power

$$S = \frac{P}{\cos \varphi} = \frac{8kW}{0.8} = 10kW$$
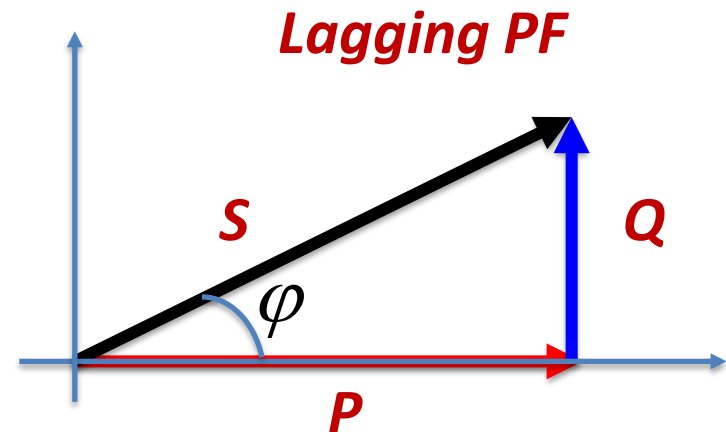
$$Q = \pm \sqrt{S^2 - P^2}$$
$$= \pm \sqrt{10^2 - 8^2} = \pm 6kVars$$



Lagging PF $Q = 6kVars$

$$S = P + jQ = (8 + 6j)kVA$$

Calculate the impedance

Recall the complex power $S = \frac{|V_{eff}|^2}{Z^*}$

$$\begin{aligned} Z &= \frac{|V_{eff}|^2}{S^*} = \frac{|240V|^2}{(8 - j6)kVA} = \frac{57.6}{8 - j6} \\ &= \frac{57.6}{10 \angle -36.87^\circ} = 5.76 \angle 36.87^\circ = 4.608 + j3.456 \end{aligned}$$

Exercise 1: use of RMS and Average P

- Problem 10.14:
a) Find the rms value of the periodic voltage shown in figure P10.14:

Figure P10.14


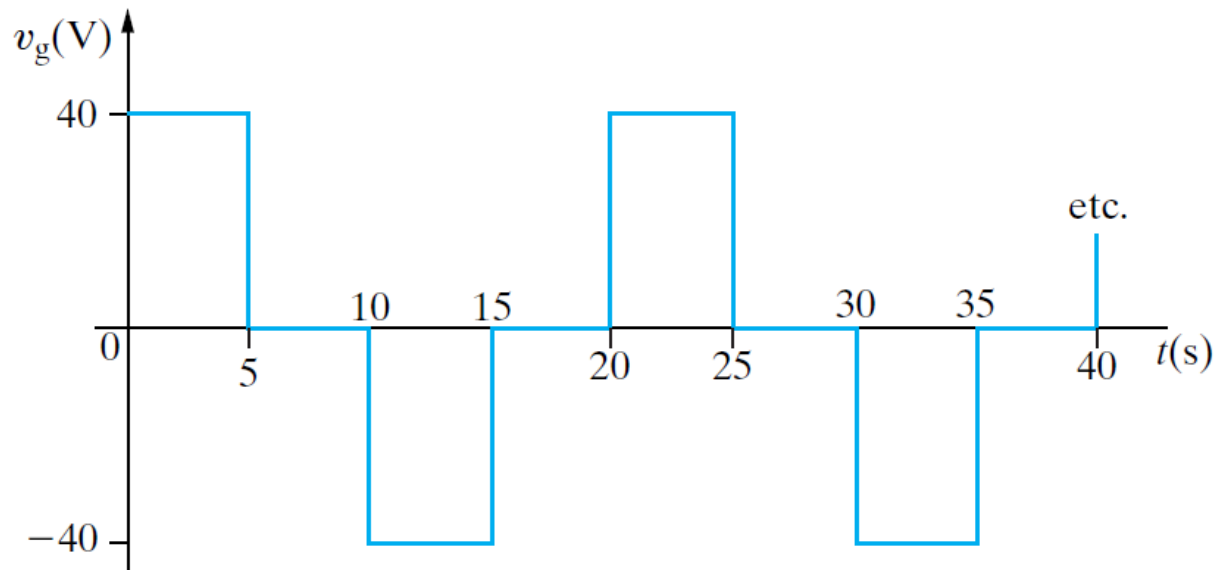


Figure P10.14

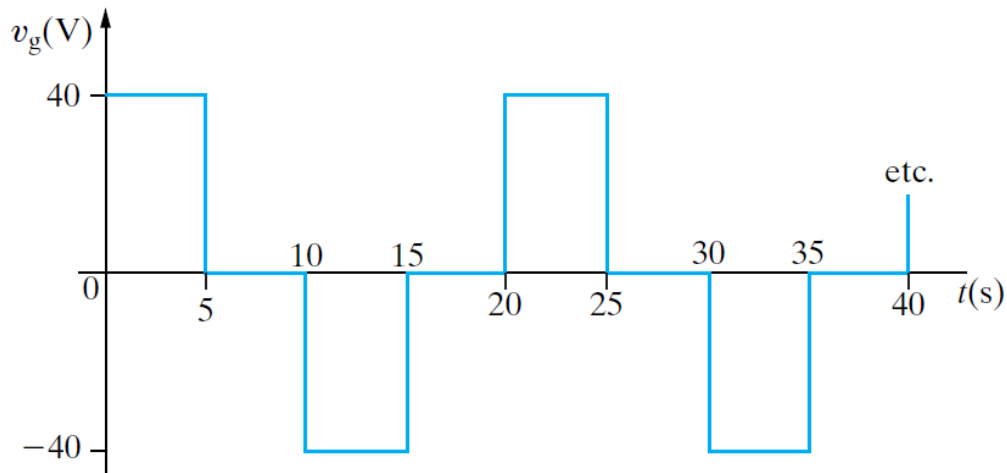


a) Find the rms value of the periodic voltage shown in figure.

$$T = 20s$$

$$\begin{aligned} V_{rms} &= \sqrt{\frac{1}{T} \int_0^T v_g^2(t) dt} = \sqrt{\frac{1}{20} \left(\int_0^5 40^2 dt + \int_{10}^{15} (-40)^2 dt \right)} \\ &= \sqrt{\frac{1}{20} \left(5 \cdot 40^2 + 5 \cdot (-40)^2 \right)} \\ &= 20\sqrt{2} \end{aligned}$$

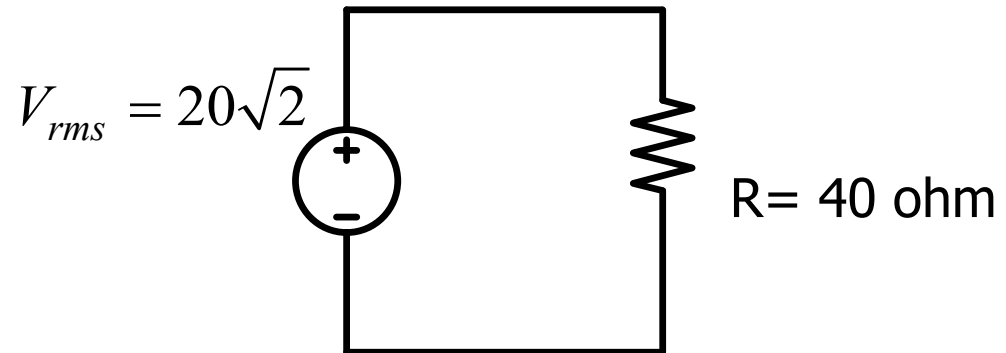b) Suppose the voltage in part a) is applied to the terminals of a 40 Ohm resistor. Calculate the average power dissipated by the resistor.

$$P = \frac{V_{rms}^2}{R} = \frac{(20\sqrt{2})^2}{40} = 20W$$



c) When the voltage in part a) is applied to a different resistor, that resistor dissipates 10 mW of average power. What is the value of the resistor?


$$R = \frac{V_{rms}^2}{P} = \frac{(20\sqrt{2})^2}{10 \times 10^{-3}} = 8 \times 10^4 \text{ ohm}$$


Exercise 2: use of Phasor

- Problem 10.20

a) Find the average power, the reactive power and the apparent power supplied by the voltage source in the circuit in figure P10.20.

Figure P10.20

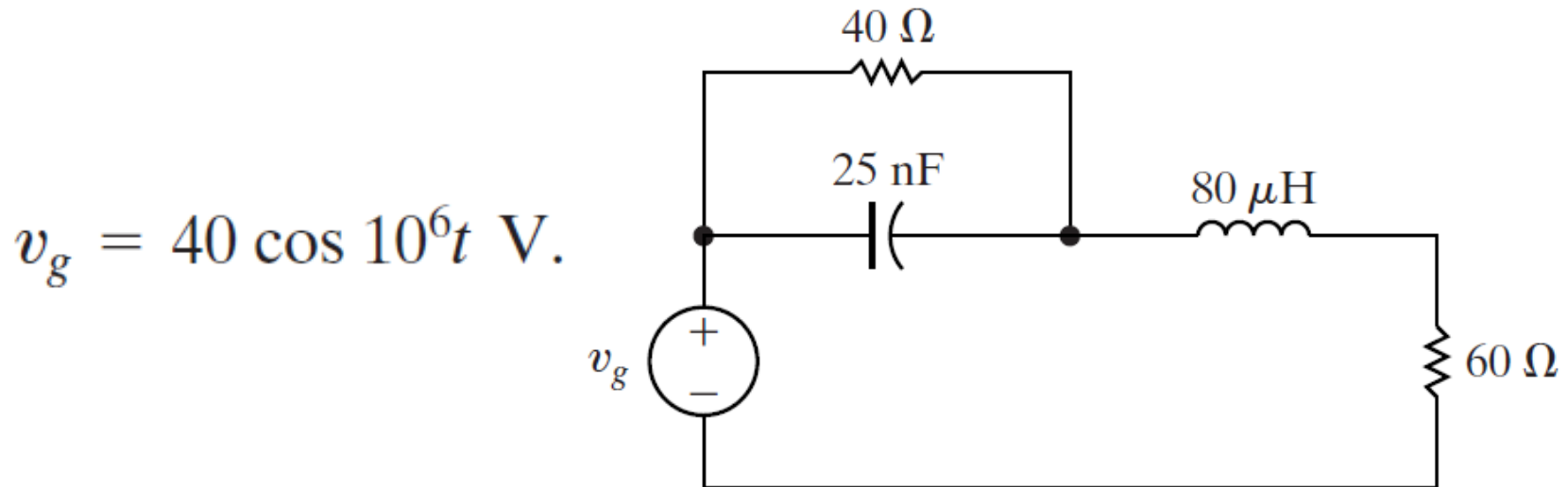

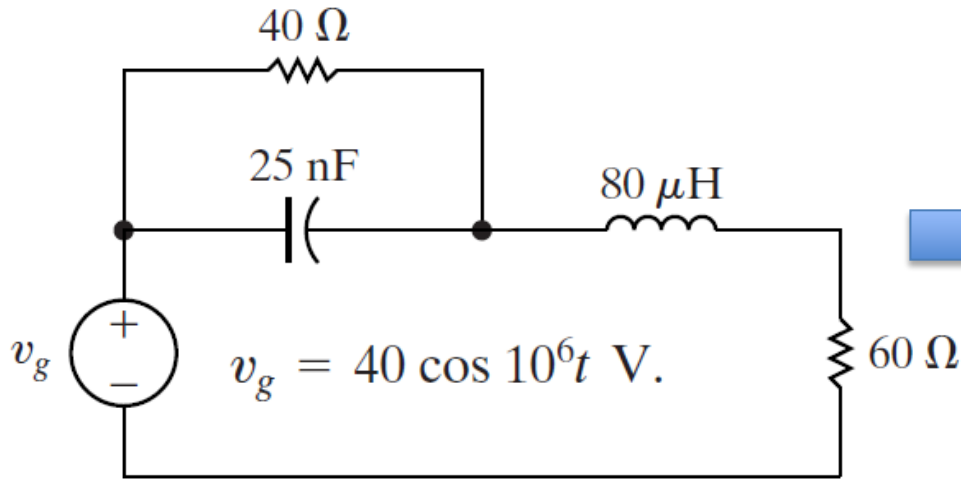


Step1:
Find out the frequency domain circuit

$$\omega = 10^6 \rightarrow$$

$$-j \frac{1}{\omega C} = \frac{-j}{25 \text{ nF} \times 10^6} = -j40 \Omega$$

$$j\omega L = j80 \mu\text{H} \times 10^6 = j80 \Omega$$


$$V_g = 20\sqrt{2}$$

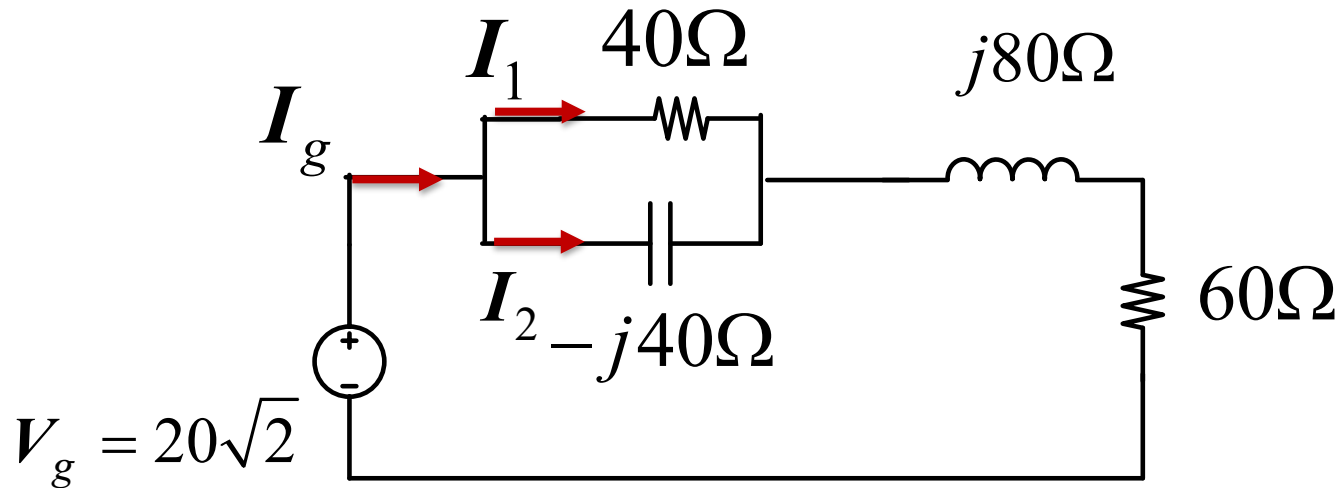

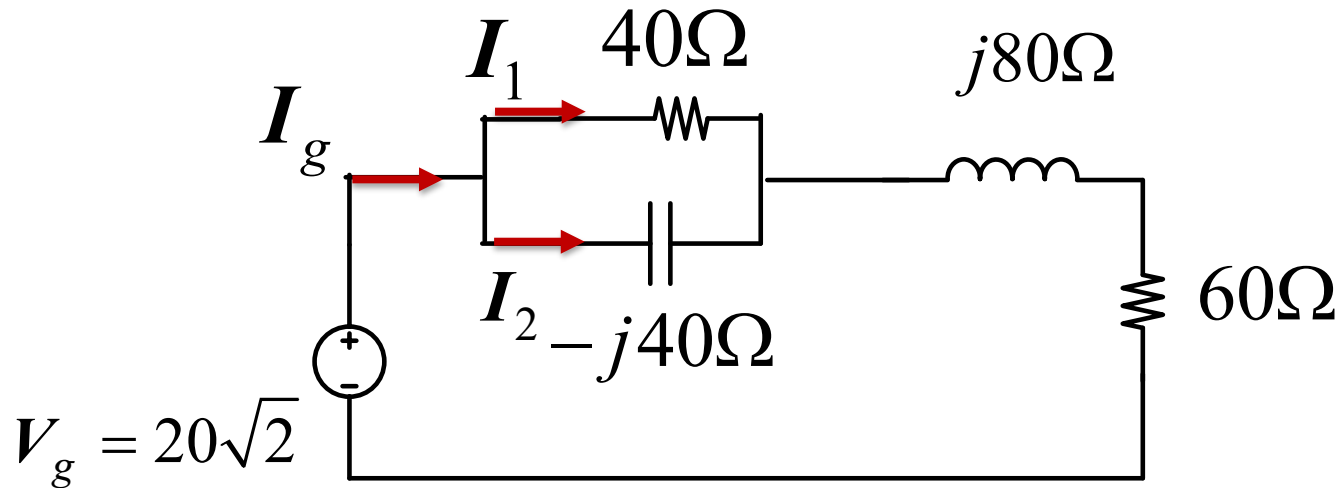a) Find the average power, the reactive power and the apparent power

Step2: Find the equivalent impedance

$$\begin{aligned} \mathbf{Z}_{eq} &= -j40\Omega \parallel 40\Omega + j80\Omega + 60\Omega \\ &= (80 + 60j)\Omega \end{aligned}$$



a) Find the average power, the reactive power and the apparent power

Solving the current phasor


$$I_g = \frac{V_g}{Z_{eq}} = \frac{20\sqrt{2}}{(80 + 60j)} = (0.226 - j0.169) A$$

Solving the complex power

$$S = V_g I_g^* = \frac{|V_g|^2}{Z_{eq}^*} = \frac{(20\sqrt{2})^2}{80 - 60j} = 8 \angle 36.8^\circ = \underbrace{(6.4)}_{P_{dev}} + \underbrace{j4.8}_{Q_{abs}} VA$$


b) Check your answer in (a) by showing
 $P_{\text{dev}} = \sum P_{\text{abs}}.$

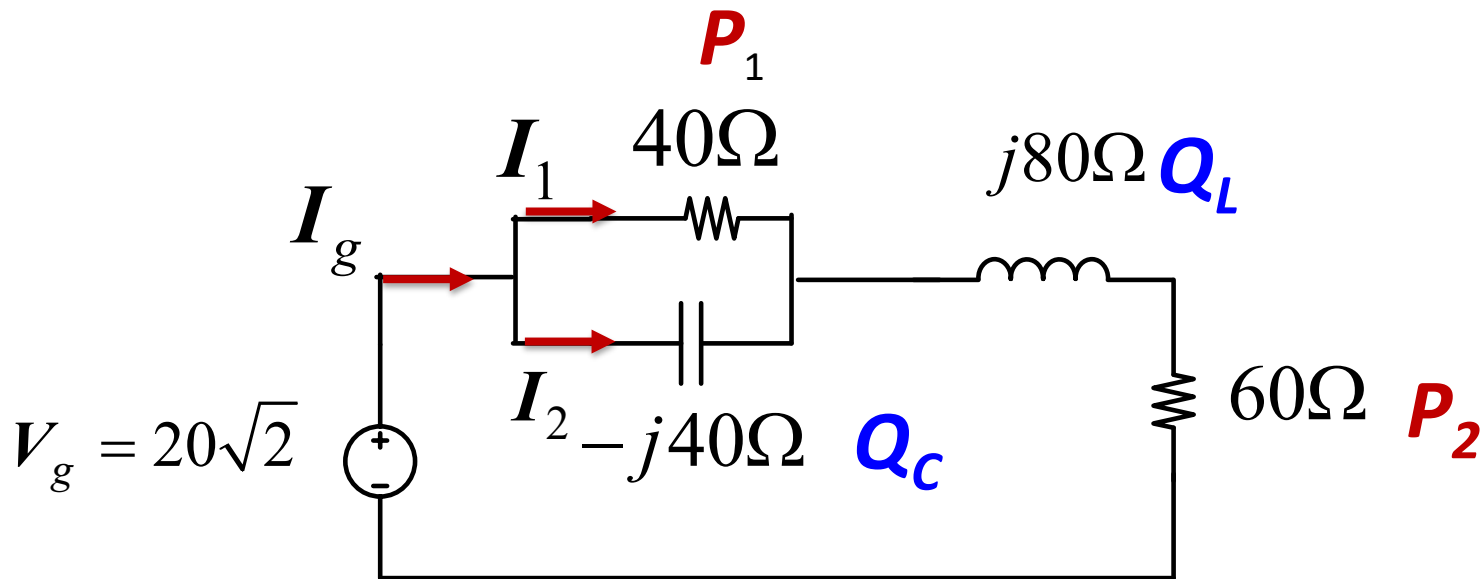c) Check your answer in (a) by showing
 $Q_{\text{dev}} = \sum Q_{\text{abs}}.$




$$P_{\text{dev}} = P_1 + P_2$$

$$Q_{\text{dev}} = Q_L + Q_C$$

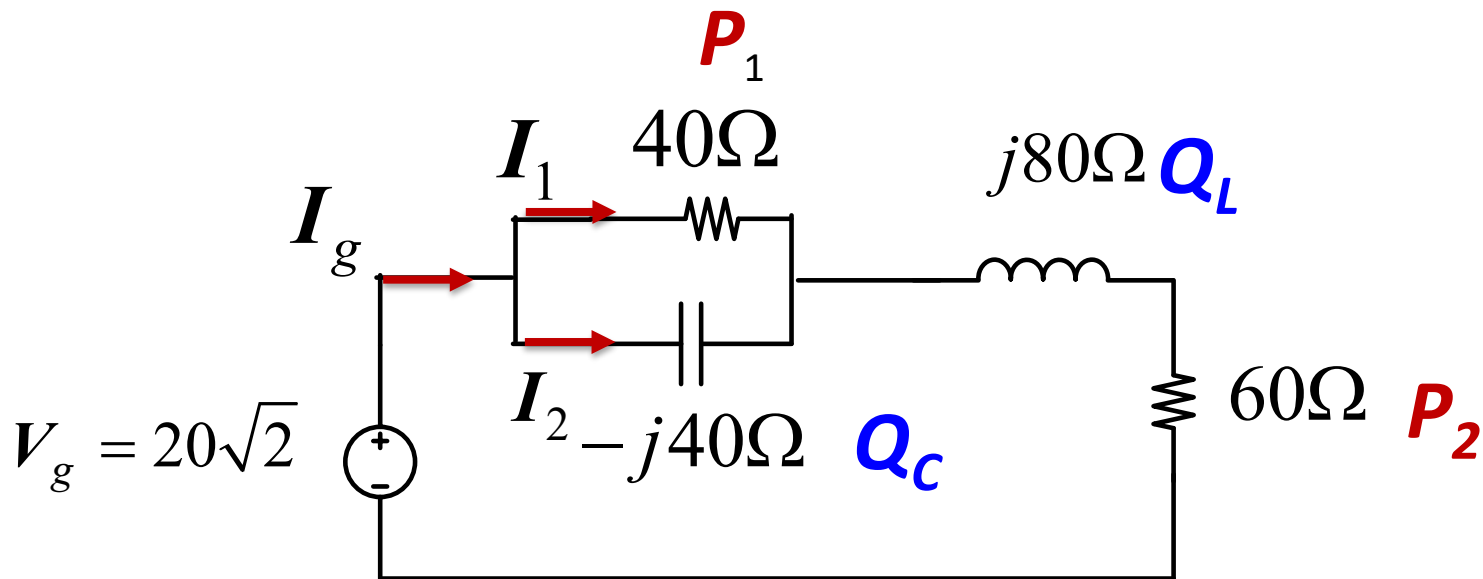

$$I_1 = I_g \frac{(-40j\Omega \parallel 40\Omega)}{40\Omega} = (0.0285 - 0.1987j) A$$
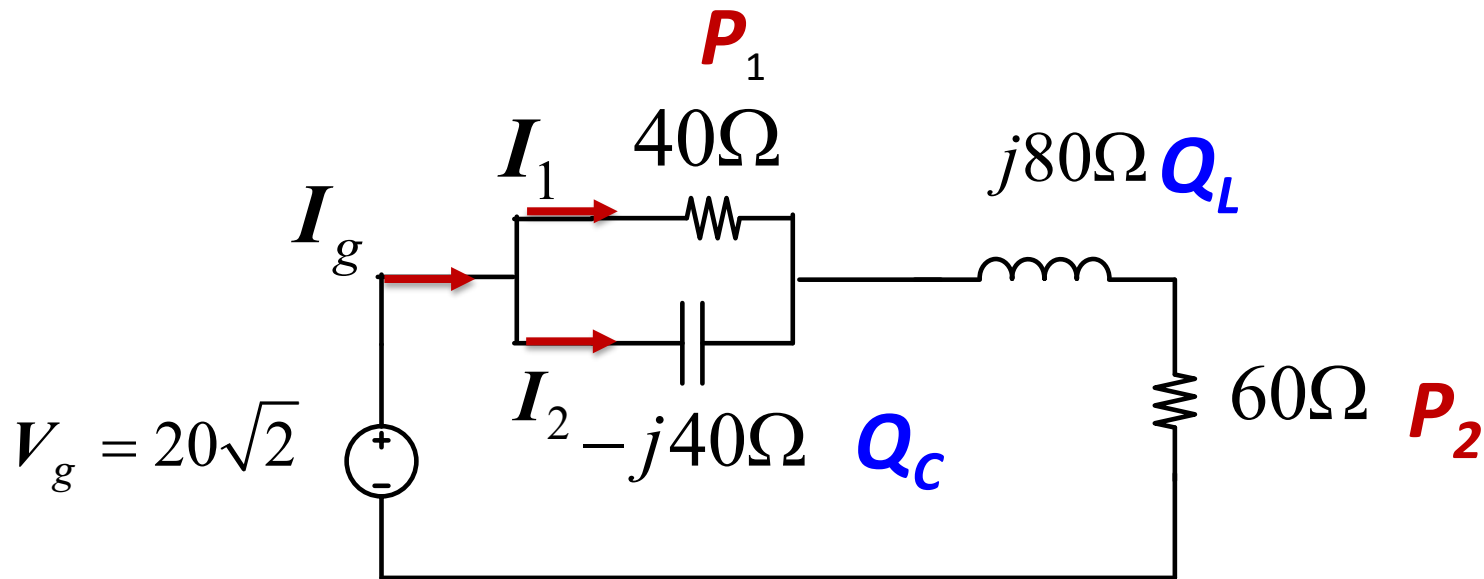
$$I_2 = I_g - I_1 = (0.1975 + 0.029j) A$$



$$P_1 + P_2 = |I_1|^2 40\Omega + |I_g|^2 60\Omega$$

$$Q_C + Q_L = -j|I_2|^2 40\Omega + j|I_g|^2 80\Omega$$


$$P_{dev} = P_1 + P_2$$

$$Q_{dev} = Q_L + Q_C$$

Homework

- P10.15
 - a) Find the rms value of the periodic voltage shown in Fig. P10.15.
 - b) If this voltage is applied to the terminals of a $4\ \Omega$ resistor, what is the average power dissipated in the resistor?

Figure P10.15

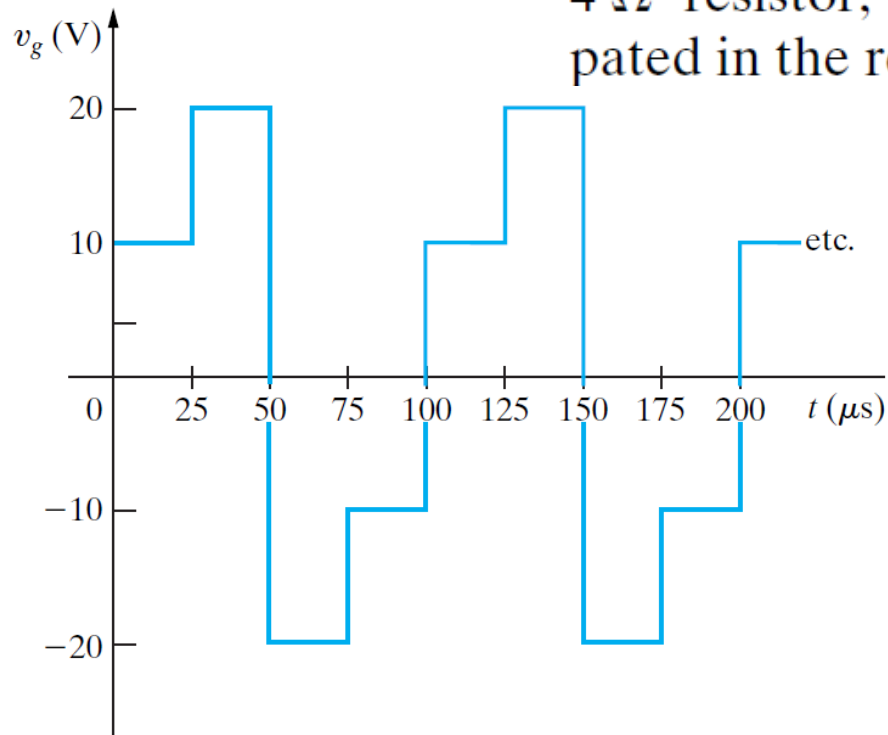

End