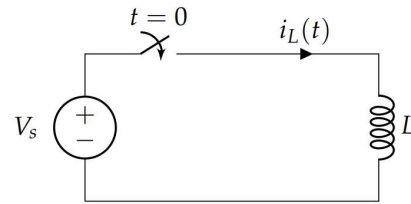


Assignment 1

torsdag 16. januar 2025 14:28

Problem 1 (Inductors and capacitors)

- (a) In the circuit on the right, $V_s = 1\text{ V}$ and $L = 1\text{ H}$. Before $t = 0$ the current through the inductor is equal to zero. At $t = 0$ the circuit is closed. Set up the differential equation for the circuit when $t \geq 0$, then calculate the current $i_L(t)$. Sketch its graph for $0 < t < 5\text{ s}$.




$$V_L = L \frac{di}{dt} \Rightarrow \frac{V_L}{L} = \frac{di}{dt}, \quad V_L = V_s = 1\text{ V}$$

$$\int \frac{di}{dt} dt = \int \frac{V_L}{L} dt$$

$$i_L(t) = \frac{V_L}{L} t + i(0) \stackrel{i_0=0}{=} t \text{ A}$$



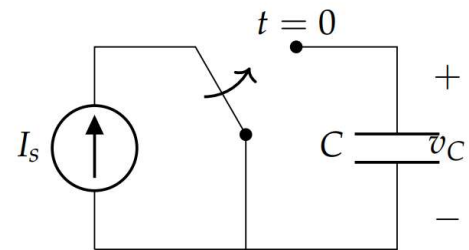- (b) The circuit on the right has a constant current source I_s . Before $t = 0$ the capacitor is energyless, i.e., $v_C(t < 0) = 0$. At $t = 0$ the switch is flipped, so that the current is forced through the capacitor C . Find the voltage $v_C(t)$ for $I_s = 1\text{ A}$ and $C = 1\text{ F}$. Sketch its graph for $0 < t < 5\text{ s}$.




$$i_C = C \frac{dv_C}{dt} \Rightarrow \frac{i_s}{C} dt = dv_C$$


$$\int 1 dv_C = \int \frac{i_s}{C} dt$$

$$v_C(t) = \frac{i_s}{C} t + v_C(0) \stackrel{v_0=0}{=} t \text{ V}$$
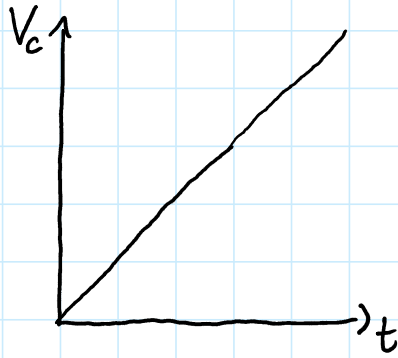
$$V_c(t) = \frac{1}{C} t + V_c(0) = t \text{ V}$$



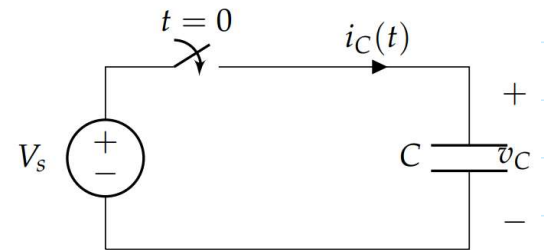- (c) Now, we will study a somewhat unrealistic circuit in order to illustrate how much a capacitor resists the change of voltage over it. The circuit on the right is closed at $t = 0$, and $V_s = 1 \text{ V}$ and $C = 1 \text{ F}$. Moreover, $v_C(t < 0) = 0$. Find the current $i_C(t)$. This is a mystical calculation. Discuss what would happen in practice.



$$i_C = C \frac{dV_C}{dt}$$

$$V_s = V_C = 1 \text{ V for } t \geq 0$$


$$\frac{dV_C}{dt} = 0 \quad \text{because } V_C \text{ is const.}$$

$$\Rightarrow i_C = 0 \quad \text{for } t > 0$$

$$\text{At } t=0 \quad i_C = \frac{dV_C}{dt} = \infty$$

In practice we should see a
a big (but not infinite) current spike
before it goes to 0.

d) Stationary equivalent:

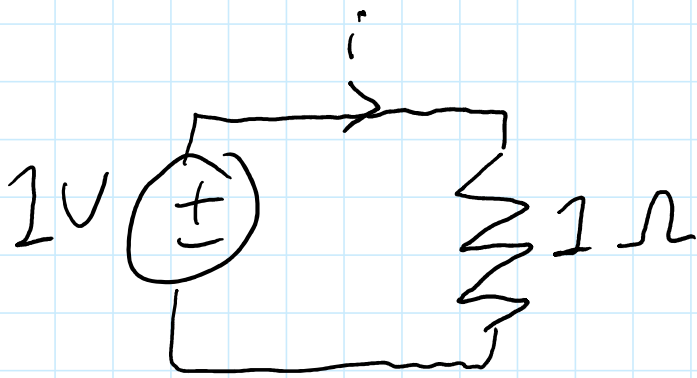

$$V = RI \Rightarrow I = \frac{V}{R} = 1A$$

e) Equivalent to open circuit:

$$i = 0A$$

d)





$$i = 1 \text{ A}$$

Problem 2

$$a) i_L(t) = \frac{V_L}{L} t + i(0) = \frac{16 \text{ V}}{100 \text{ mH}} \cdot t = 160 \cdot t \text{ A}$$

for $0 \leq t \leq 10 \text{ ms}$

$$b) i_L\left(\frac{1}{100}\right) = 160 \cdot \frac{1}{100} \text{ A} = 1,6 \text{ A}$$

$$10 \text{ ms} \leq t \leq T:$$

$$i_L\left(\frac{1}{100}\right) = 1,6 \text{ A} = \frac{-5 \text{ V}}{100 \text{ mH}} \cdot \frac{1}{100} + C \text{ A}$$


$$C = 2,1$$

$$\Rightarrow i_L(t) = -50 \frac{\text{V}}{\text{H}} \cdot t + 2,1 \text{ A}$$

$$i_L(T) = -50 \frac{\text{V}}{\text{H}} \cdot t + 2,1 \text{ A} = 0$$

2,1

$$T = \frac{2,1}{50} \text{ s} = 0,042 \text{ s} = 42 \text{ ms}$$

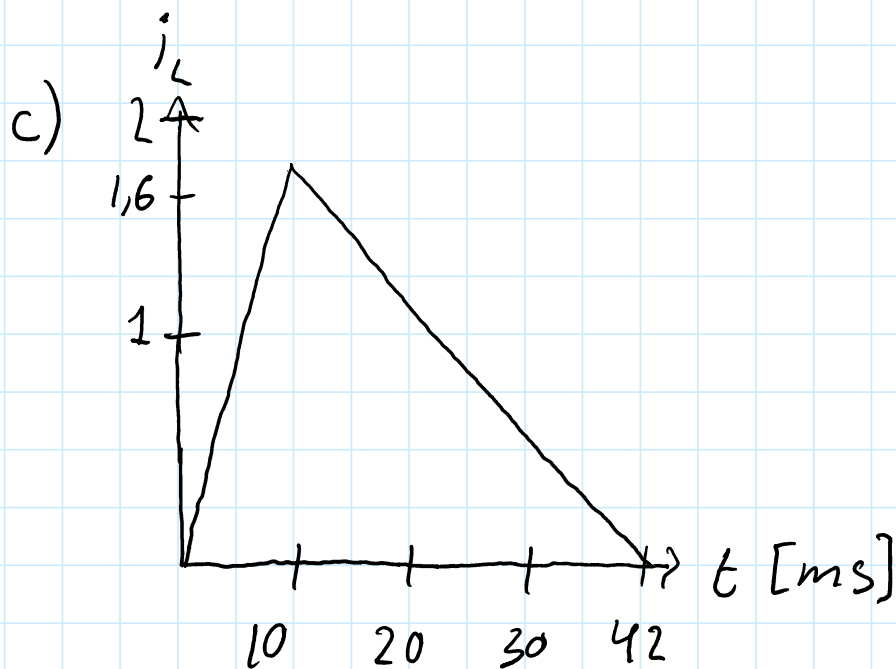

Problem 3

a/b $V_s = V_R + V_L$

$$V_s = R i_L + L \frac{di_L}{dt}$$

$$i_L(t) = C e^{-\frac{R}{L}t} + \frac{V_s}{R}$$

$$i_L(0) = C + \frac{V_s}{R} = 0 \Rightarrow C = -\frac{V_s}{R}$$

$$i_L(t) = \frac{V_s}{R} [1 - e^{-\frac{R}{L}t}]$$

$$i_L(\infty) = \frac{V_s}{R}$$

c) $i_L(0^-) = 0$ because it's an open circuit

$i_L(0^+) = 0$ because current lags

voltage / inductors resist change in current

$$d) i_L(t) = \frac{V_s}{R} \left[1 - e^{-\frac{R}{L}t} \right]$$


$$V_s = 1V \quad R = 1\Omega \quad L = 0,02H \text{ or } 0,2H$$

$$L = 0,02H :$$

$$\underline{i_L(t) = 1 - e^{-50t}}$$

$$L = 0,2H$$

$$\underline{i_L(t) = 1 - e^{-5t}}$$

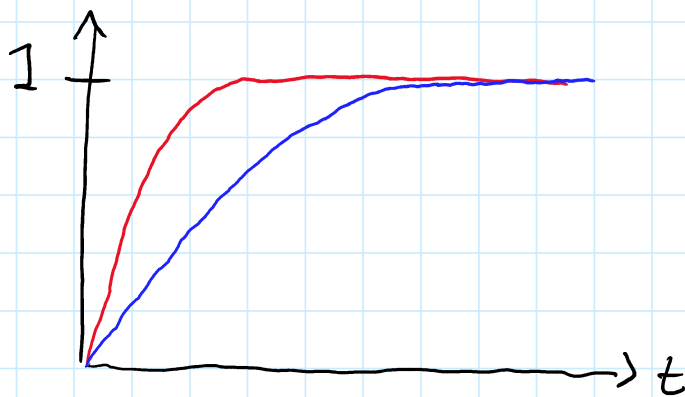

The current changes more slowly with more Henry. Both expressions converge to $\frac{V_s}{R}$.

Problem 4

$$a) V_L = L \frac{di_L}{dt}$$

$$\text{Using } \mathcal{L}\{f'(t)\} = sF(s) - f(0):$$

$$\mathcal{L}\{V_L\} = \mathcal{L}\left\{L \frac{di_L}{dt}\right\}$$

$$V_L(s) = sL I_L(s) - Li_L(0)$$

$$b) V_S = R \cdot i_L + L \frac{di_L}{dt}$$

$$\frac{V_S}{s} = R I_L(s) + sL I_L(s) - \underbrace{Li_L(0)}_0$$

$$I_L(s) = \frac{\frac{V_S}{s}}{R + sL}$$

$$i_L(t) = \frac{V_S}{L} \cdot \mathcal{L}^{-1}\left\{\frac{1}{s(s + \frac{R}{L})}\right\}$$

Partial fractions:

$$\frac{1}{s(s + \frac{R}{L})} = \frac{\frac{L}{R}}{s} - \frac{\frac{L}{R}}{s + \frac{R}{L}}$$

$$1 \quad , \quad 1 \quad , \quad \frac{L}{R} \quad , \quad 1 \quad , \quad \frac{R}{L} t$$

$$\mathcal{L}\left\{\frac{\frac{L}{R}}{s}\right\} = \frac{L}{R} \quad \text{and} \quad \mathcal{L}\left\{-\frac{\frac{L}{R}}{s + \frac{R}{L}}\right\} = -\frac{L}{R} e^{-\frac{R}{L}t}$$

$$\begin{aligned} i_L(t) &= \frac{V_S}{L} \cdot \left[\frac{L}{R} - \frac{L}{R} e^{-\frac{R}{L}t} \right] \\ &= \frac{V_S}{R} \left[1 - e^{-\frac{R}{L}t} \right] \end{aligned}$$

$$\begin{aligned} c) \quad i_c(t) &= C \frac{dV_c(t)}{dt} \\ I_c(s) &= \mathcal{L}\left\{C \frac{dV_c(t)}{dt}\right\} \\ &= CsV_c - CV_c(0) \end{aligned}$$

$$d) \quad V_c = V_R = Ri_c(t)$$

$$V_c - Ri_c(t) = 0$$

$$V_c - RC \frac{dV_c}{dt} = 0$$

$$\frac{V_c}{R} - C \frac{dV_c}{dt} = 0, \quad \frac{dV_c}{dt} = \frac{d}{dt}(R \cdot i_c(t))$$


$$i(t) - RC \frac{di_c(t)}{dt} = 0$$

$$e) \quad I(s) = RCsI(s) - RCi(0), \quad i(0) = \frac{V_0}{R}$$

$$e) I(s) = RCs I(s) - RC i(0), \quad i(0) = \frac{V_0}{R}$$

$$I(s) = \frac{-RC \frac{V_0}{R}}{1 - RCs} = \frac{\frac{V_0}{R}}{s - \frac{1}{RC}}$$

$$i_c(t) = \frac{V_0}{R} e^{\frac{1}{RC}t} \leftarrow \text{Should be a minus}$$

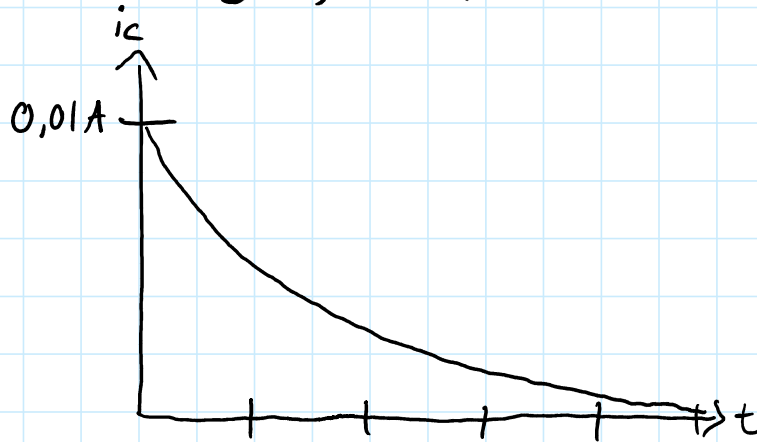

Problem 5

$$a) \frac{V_s}{R} \left[1 - e^{-\frac{R}{L}t} \right] = \frac{V_s}{R} \left(1 - \frac{1}{e} \right)$$

$$e^{-\frac{R}{L}t} = e^{-1} \Rightarrow t = \frac{L}{R} = \tau$$

$$b) i_c(t) = \frac{V_0}{R} e^{-\frac{t}{RC}}$$

$$i_c(\tau) = \frac{V_0}{R} e^{-\frac{\tau}{RC}} = \frac{V_0}{RC} \cdot 1 - \left(1 - \frac{1}{e} \right)$$

$$\Rightarrow e^{-\frac{\tau}{RC}} = e^{-1} \Rightarrow \tau = RC$$

$\nearrow 20 \frac{V}{\mu s}$

