

Assignment 6

lørdag 22. februar 2025

14:23

Problem 1

a) Ohm's law: $Z_L = \frac{V_L}{I_L}$ and $V_L = 132000 \underline{V}$

Complex power: $S_L = V_L \cdot \overline{I_L} \Rightarrow \overline{I_L} = \frac{S_L}{V_L}$

$$S_L = 50 \angle 36,87^\circ \text{ MVA} = 50 \cdot 10^6 \angle 36,87^\circ \text{ VA}$$

$$\overline{S_L} = 50 \cdot 10^6 \angle -36,87^\circ$$

$$\overline{I_L} = \frac{50 \cdot 10^6 \angle -36,87^\circ \text{ VA}}{132000 \text{ V}} = 378,78 \angle -36,87^\circ \text{ A}$$

$$Z_L = \frac{132000 \text{ V}}{378,78 \angle -36,87^\circ \text{ A}} = 348,4 \angle 36,87^\circ \Omega$$

Alternatively: $S_L = \frac{V_L^2}{Z_L} \Rightarrow Z_L = \frac{V_L^2}{S_L}$

Power factor: $\text{pf} = \cos(\phi_{PF}) = \cos(36,87^\circ) = 0,8$

Positive pf $\Rightarrow$ Current lags voltage

b) See task a)

c) KVL: $V_S = V_L + \underbrace{I_L \cdot Z_{\text{line}}}_{V_{\text{line}}}$

$$Z_{\text{line}} = R_{\text{line}} + jX_{\text{line}} = (10 + 35j) \Omega$$

$$Z_{\text{line}} = 36,4 \angle 74,05^\circ$$

$$Z_{\text{line}} = 36,4 \angle 74,05^\circ$$

$$V_{\text{line}} = I_L \cdot Z_{\text{line}} = 378,79 \angle -36,87^\circ \cdot 36,4 \angle 74,05^\circ = 13788 \angle 36,18^\circ \text{ V}$$

$$V_S = V_L + V_{\text{line}} = 132000 \angle 0^\circ + 13788 \angle 36,18^\circ$$

Cartesian:

$$V_{\text{line}} = (11000 + 8320j) \text{ V} \quad \text{and} \quad V_L = 132000$$

$$V_S = 132000 + 11000 + 8320j = 143000 + 8320j$$

$$|V_S| = \sqrt{143000^2 + 8320^2} = 143241 \text{ V}$$

$$\angle V_S = \tan^{-1} \left(\frac{8320}{143000} \right) = 3,33^\circ$$

$$V_S = 143241 \angle 3,33^\circ \text{ V}$$


$$d) S = V_S \cdot \overline{I_L} = 143230 \angle 3,33^\circ \cdot 378,79 \angle -36,87^\circ$$

$$= 54,25 \angle 40,2^\circ \text{ MVA}$$

$$P = |S| \cos(\varphi_{pf}) = 54,22 \cdot 10^6 \cos(40,2^\circ) = 41,44 \text{ MW}$$

$$Q = |S| \sin(\varphi_{pf}) = 54,22 \cdot 10^6 \sin(40,2^\circ) = 35,02 \text{ MVar}$$

e)

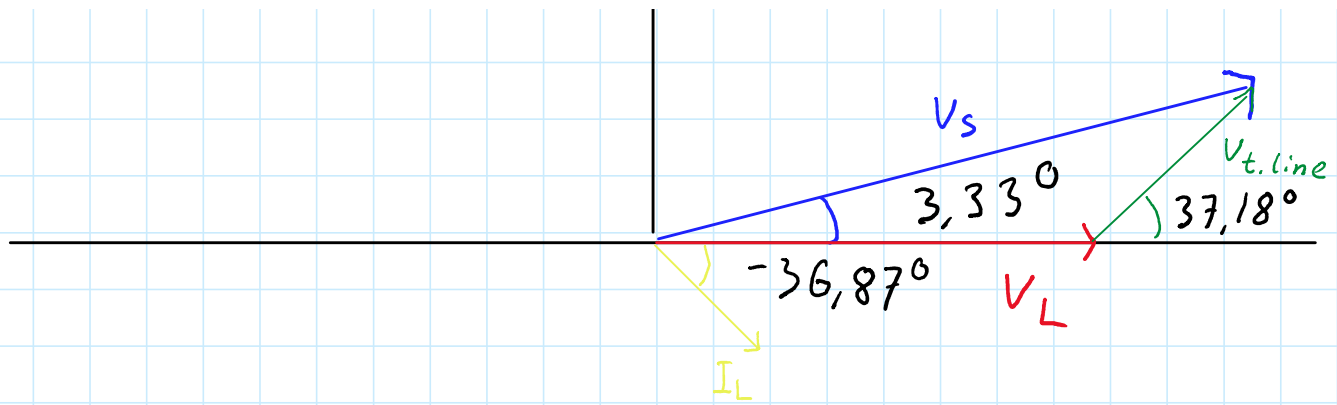

Problem 2

a) $V_L = V_S = 22000 \text{ V}$

b) $P = S_L \cos(\varphi) \Rightarrow |S| = \frac{P}{\cos \varphi} = \frac{5 \cdot 10^6}{0,9} = 5,556 \text{ MVA}$

$$\varphi = \cos^{-1}(0,9) = 25,84^\circ$$

$$S_L = 5,556 \angle 25,84^\circ \text{ MVA}$$

$$Z_L = \frac{V_L^2}{S}, \quad \bar{S} = 5,556 \angle -25,84^\circ \text{ MVA}$$

$$Z_L = \frac{(22000)^2}{5,556 \cdot 10^6 \angle -25,84^\circ} = 87,05 \angle 25,84^\circ \Omega$$

c) $|S| = \frac{P}{\cos \varphi} = 5,56 \text{ MVA}$

$$I_L = \frac{|S|}{V_L} = \frac{5,56 \cdot 10^6}{22000} = 252,73 \text{ A} \quad \text{and} \quad \varphi = 25,84^\circ$$

$$I_L = 252,73 \angle -25,84^\circ \text{ A}$$

$$V_{\text{drop}} = I_L \cdot jX_{\text{line}} = 252,73 \angle -25,84^\circ \cdot 10 \angle 90^\circ$$

$$= 2527,3 \angle 64,16^\circ$$

$$V_S = V_L + V_{\text{drop}} = 22000 + 2527,3 \angle 64,16^\circ$$

$$|V_S| = 22710 \text{ V}$$

$$V_S - V_L \cdot V_{drop} = 22000 \cdot 2027,5267,16$$

$$|V_S| = 23219,2 \text{ V}$$

$$\text{Percentage drop} : \frac{23219,2 - 22000}{23219,2} \cdot 100 = 5,21\%$$

$$d) \text{ Voltage drop} : V_{drop} = I_L \cdot jX_{line}$$

Reducing reactive power $\rightarrow$ current $\downarrow \rightarrow$ Voltage $\downarrow$

Capacitor on land: Line still carries full reactive current

$$e) Q_L = \sqrt{S^2 - P^2} = 2,43 \cdot 10^6 \text{ VAR}$$

$$Q_C = V_L^2 \cdot \omega C_L \text{ where } \omega = 2\pi f \text{ and } f = 50 \text{ Hz}$$

$$Q_C = 15,94 \mu\text{F}$$

$$f) V_{drop} = I_L \cdot jX_{line} \text{ where } X_{line} = 10 \Omega$$

Current is real (no phase shift)

$$I_L = \frac{P}{V_L} = \frac{5 \cdot 10^6}{22000} \text{ A} = 227,27 \text{ A}$$

$$V_{drop} = 227,27 \cdot j10 \Rightarrow |V_{drop}| = 2272,7 \text{ V}$$

$$V_L = V_S - V_{drop} = 22000 - j2272,7$$

$$|V_L| = 22116,4 \text{ V}$$

$$\frac{V_S - V_L \cdot 100}{22000} = \frac{-116,4}{22000} = -0,53\%$$

Problem 3

$$a) V_{th} = 240 \text{ V}$$

$$V_{ab} = \frac{Z_L}{Z_L + R_{th} + jX_{th}} \Rightarrow V_{ab} = \frac{30 - 30j}{(30 + R_{th}) + (X_{th} - 30)j} V_{th}$$

$$144 \angle -36,86^\circ = \frac{94,87 \angle -18,43}{r \angle \theta} \cdot 240$$

$$r \angle \theta = 158,117 \angle 18,43$$

$$R_{th} = 60, \quad X_{th} = 80$$

b) Skip

$$c) Z_L = 60 - 80j$$

$$S = \frac{240^2 \cdot (60 - 80j)}{120^2} = 240 - 320j$$